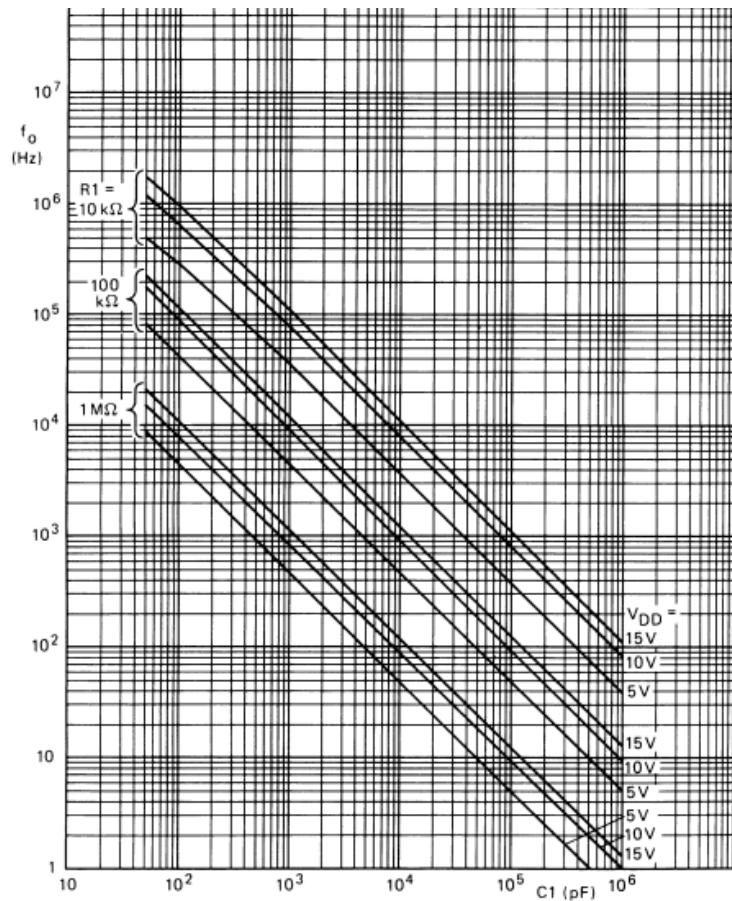



## Devoir 4




1. Selon la figure 7,  $f_0 \approx 85\text{kHz}$ ,  $f_{\max} = 2f_0 = 170\text{kHz}$ , PLAGE = 170kHz.

2.

$V1=0\text{v}$ :

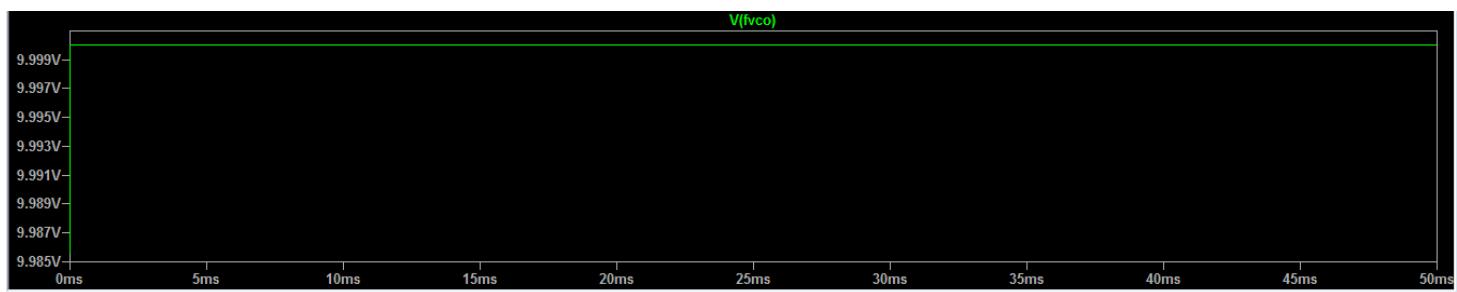


$V1=1\text{v}$ :

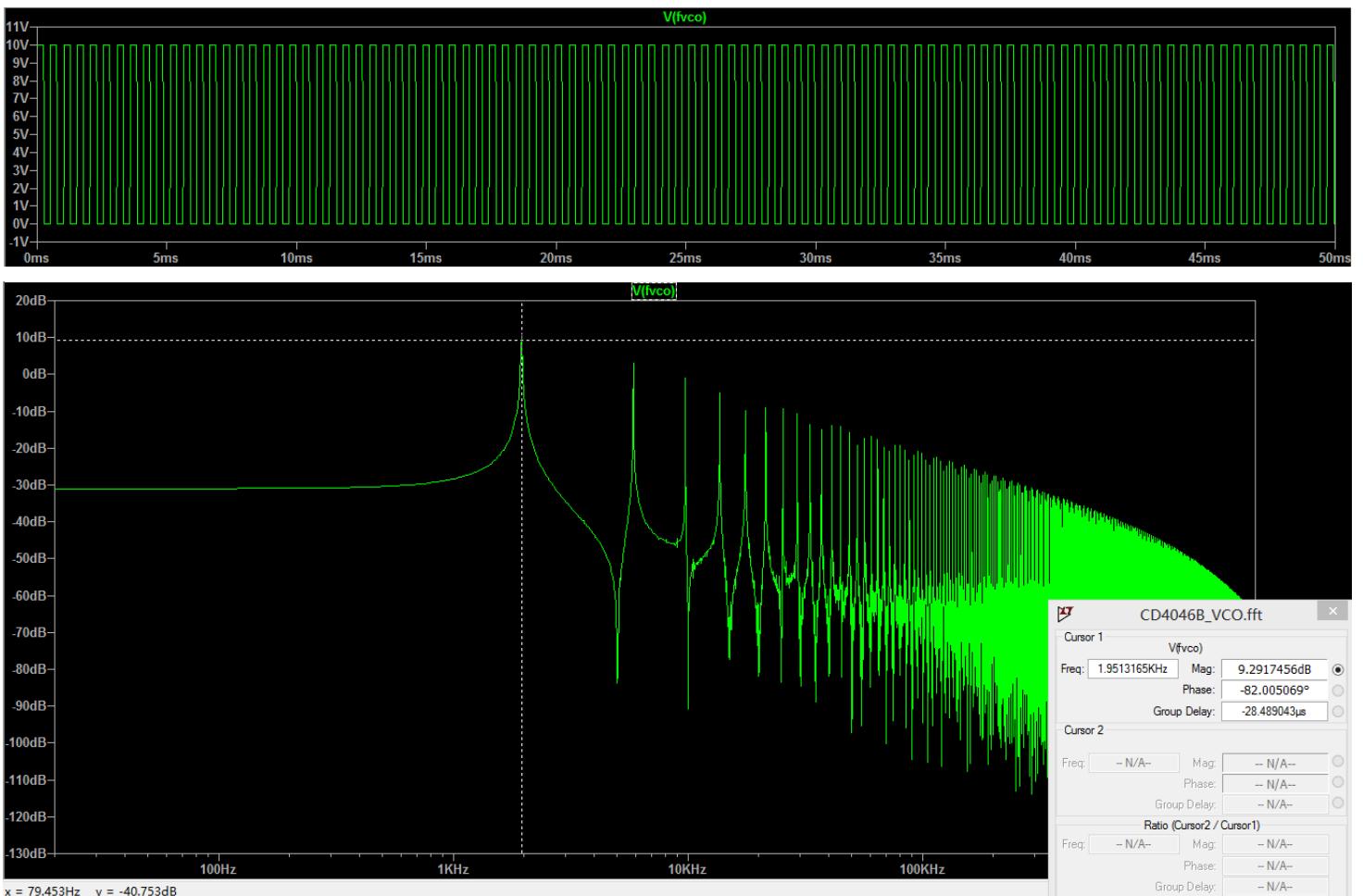


$$F=1.95\text{kHz}, G=9.29\text{db}.$$

V=2:

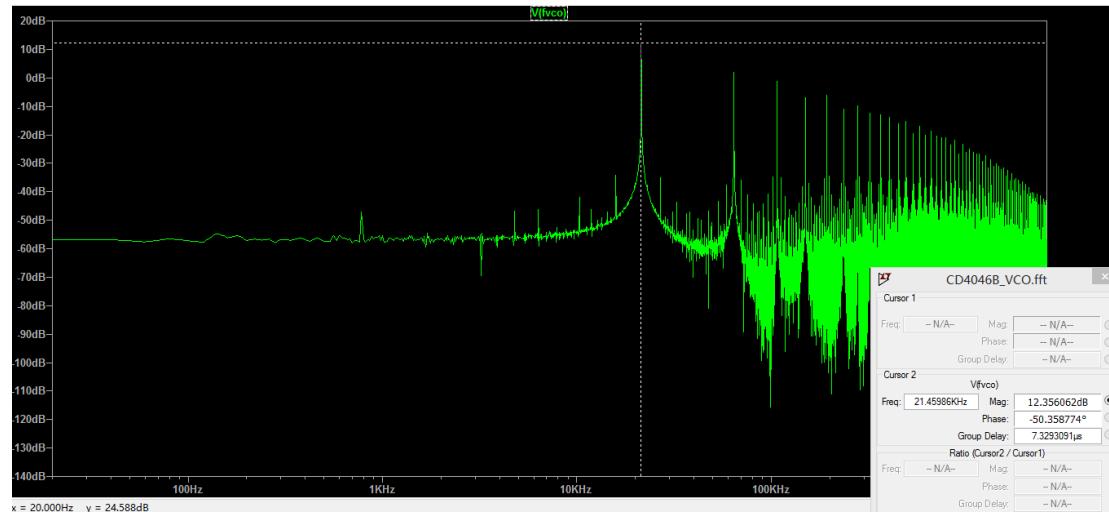


F=21.46khz,G=12.36db.

V=3:

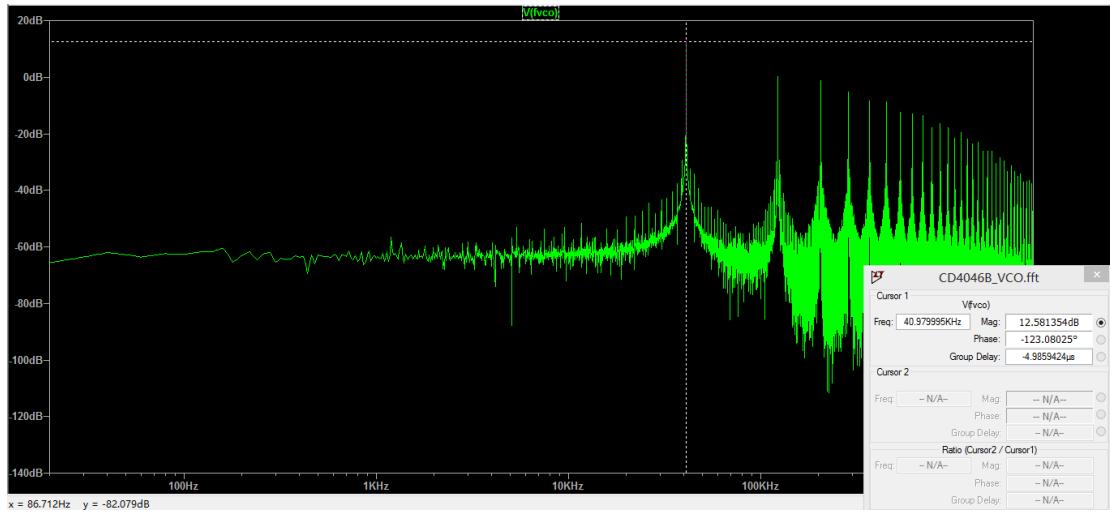


F=40.98khz,G=12.58db.

V=4:

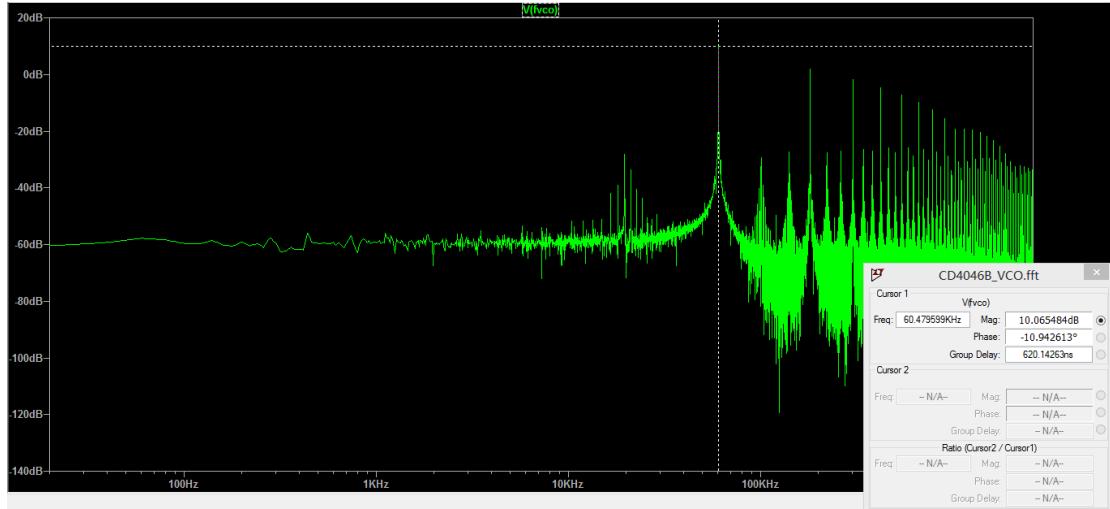


F=60.48khz,G=10.07db.

V=5:

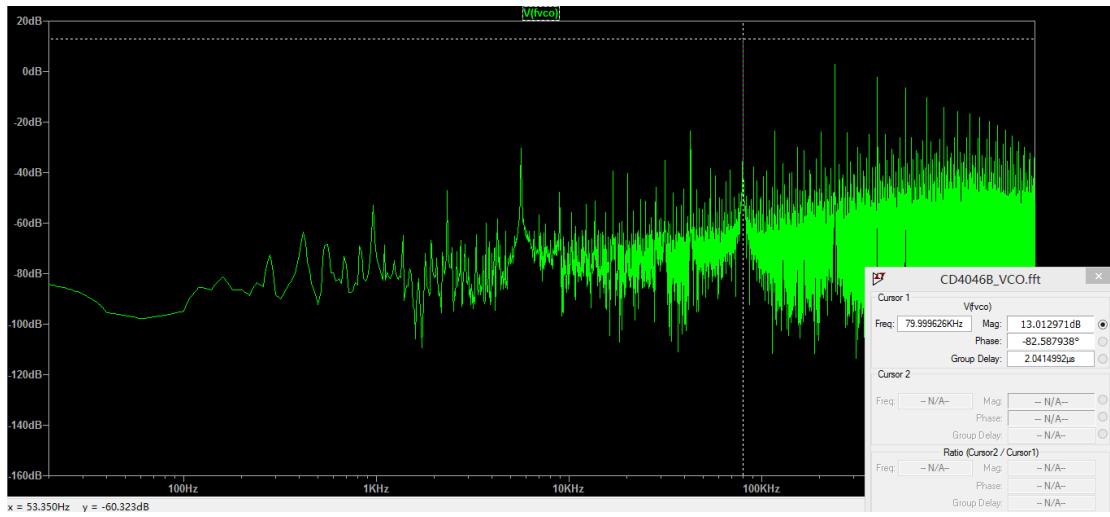


F=80.00khz,G=13.01db.

V=6:

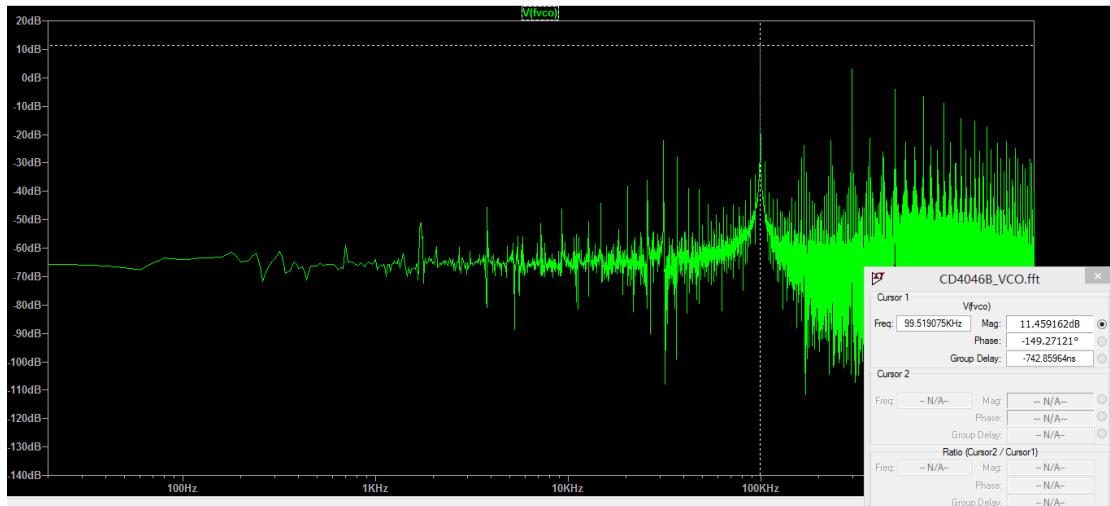


F=99.52khz,G=11.46db.

V=7:

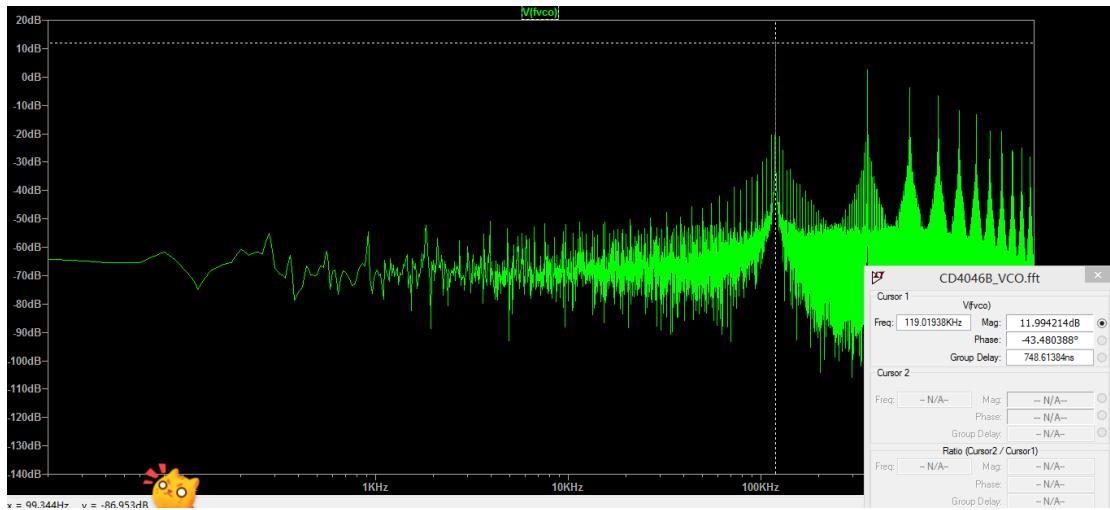


F=119.02kHz, G=11.99db.

V=8:

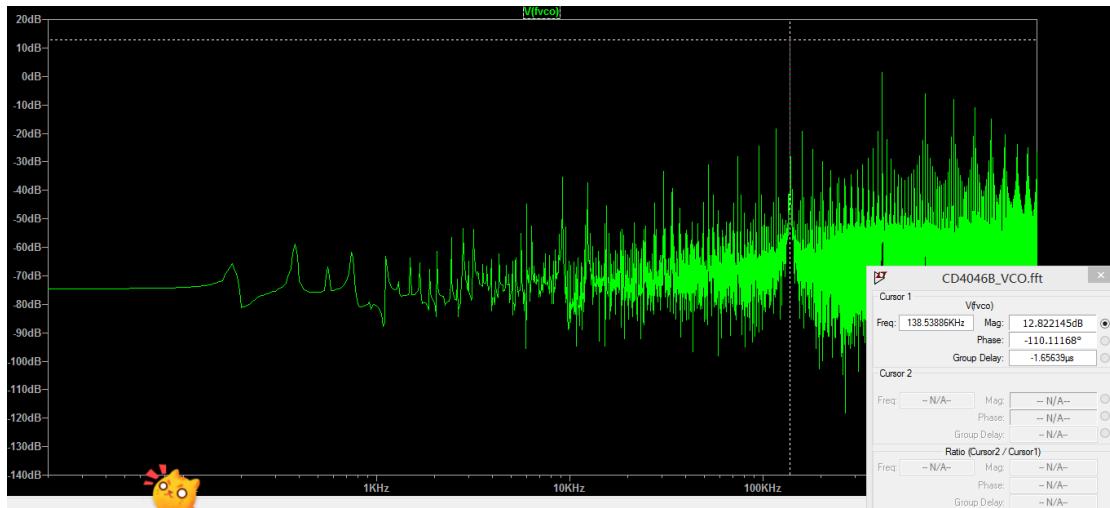


F=138.54kHz, G=12.82db.

V=9:

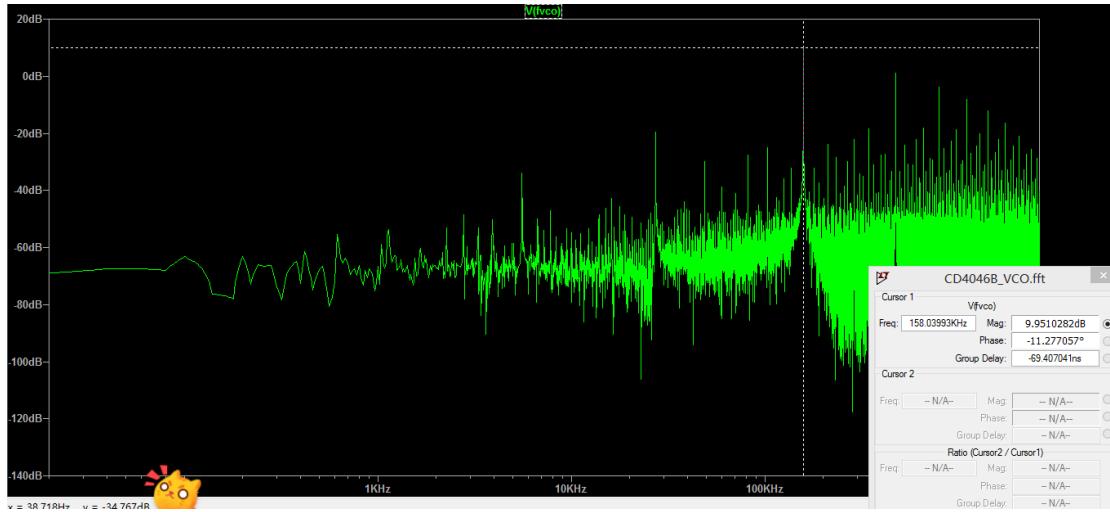


F=158.04kHz, G=9.95db.

V=10:

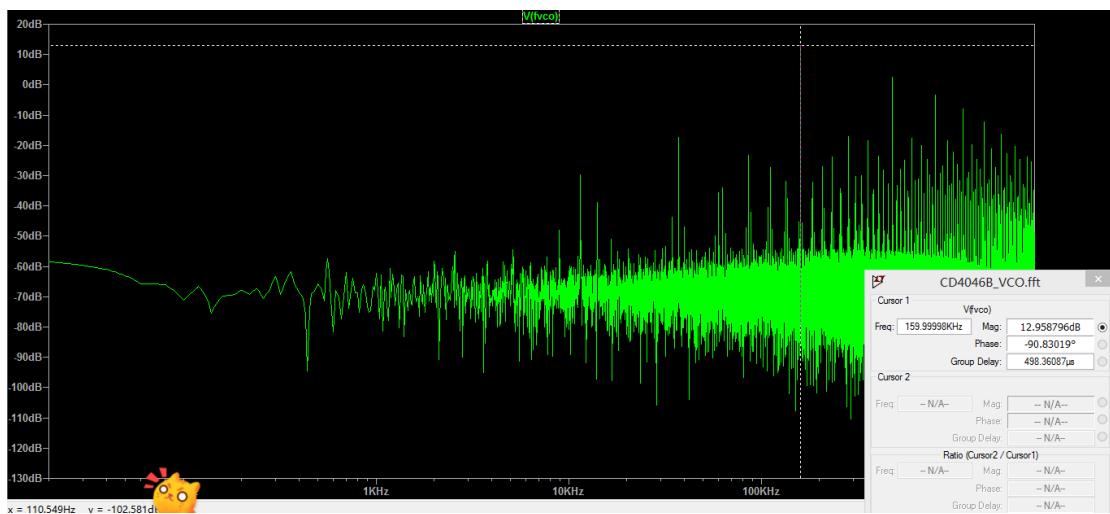

F=160.00kHz, G=12.96db.

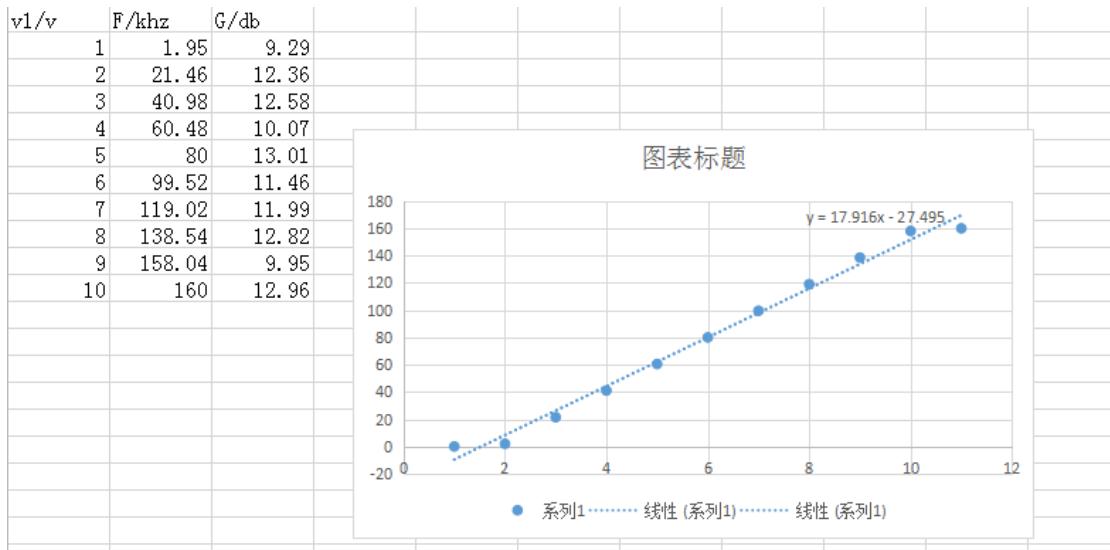


En utilisant Excel, on peut voir que la relation entre F et v1 est presque linéaire (sauf entre [0,1] et [9,10]). Fmax=160, qui est le même que le modèle  $0.16 \times 10^6$ .


3.

(1)Pc2

C2=100nF:

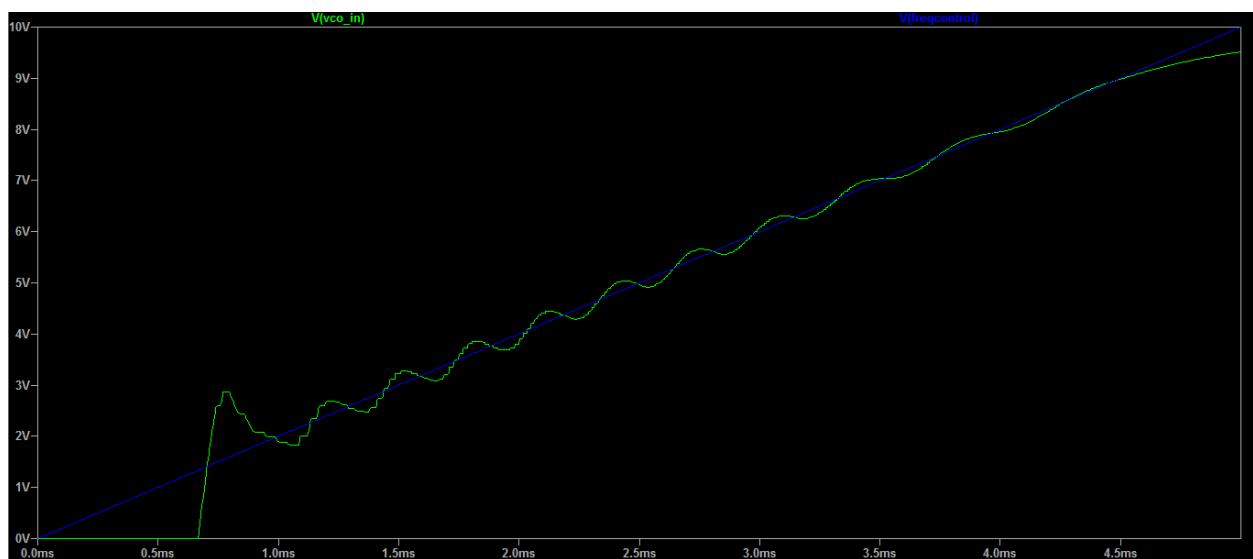


C2=10F:

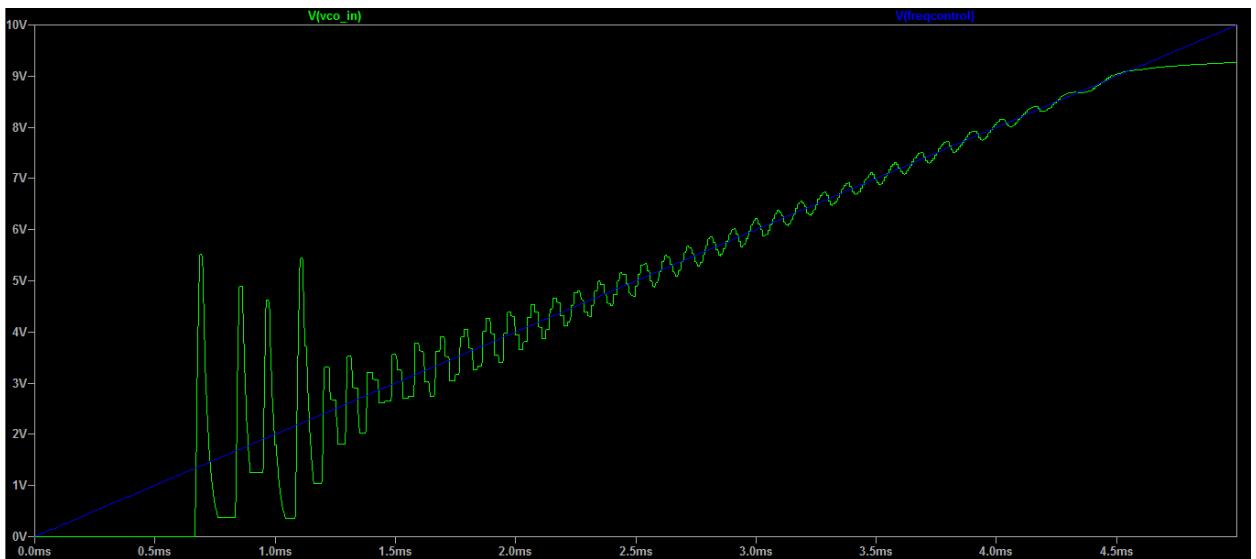


(2)Pc1

C2=100nF:

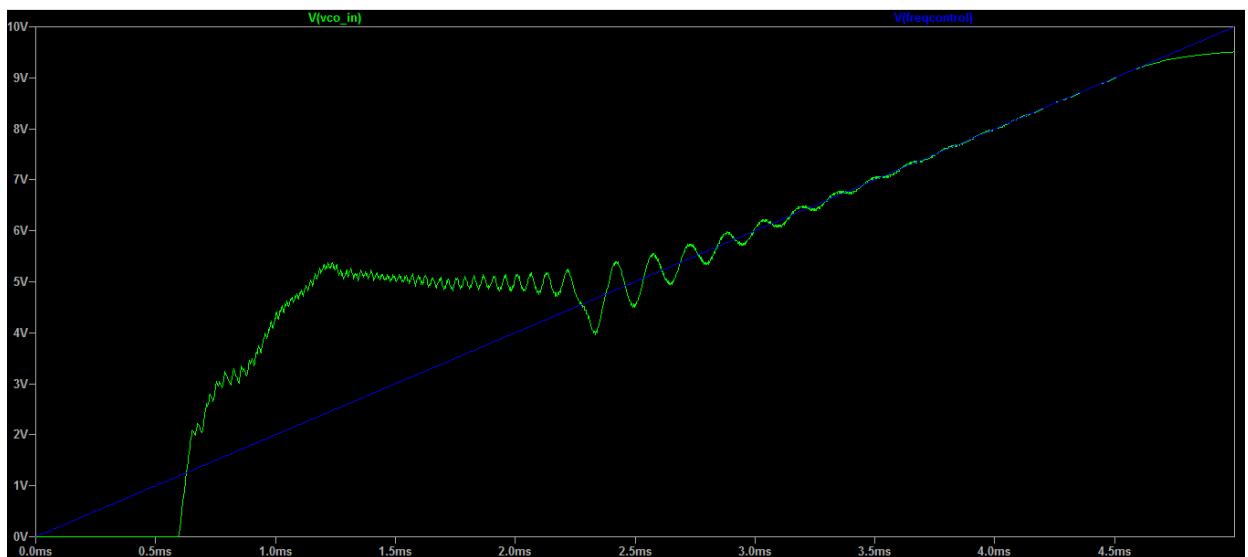


C2=10nF:

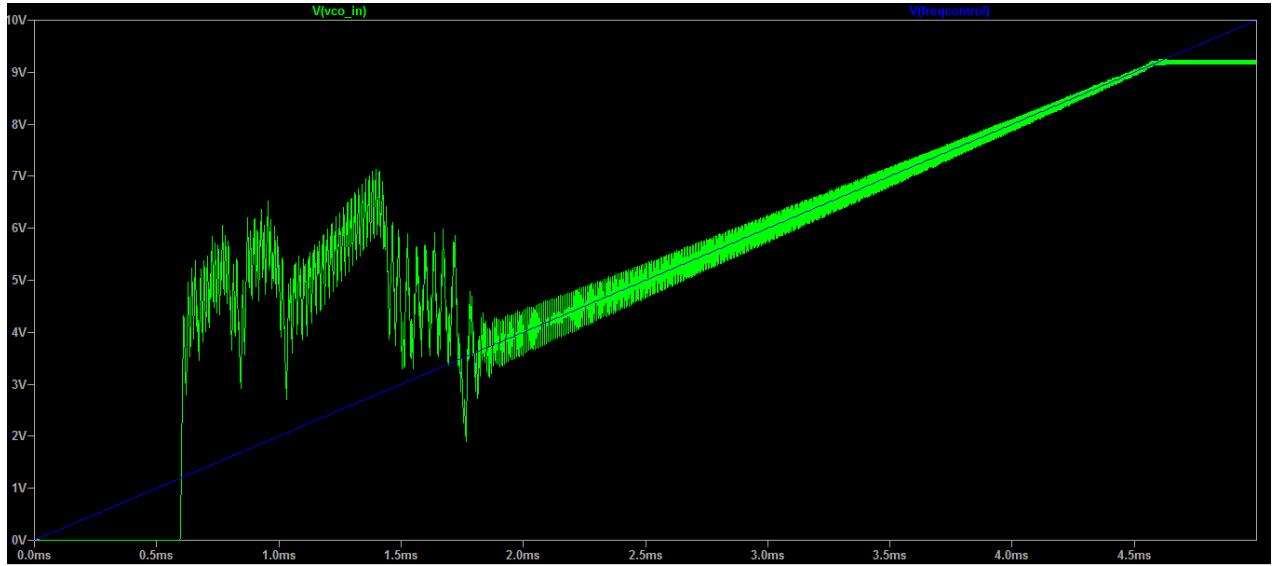


4.

(1)Pc2

C2=100nF:

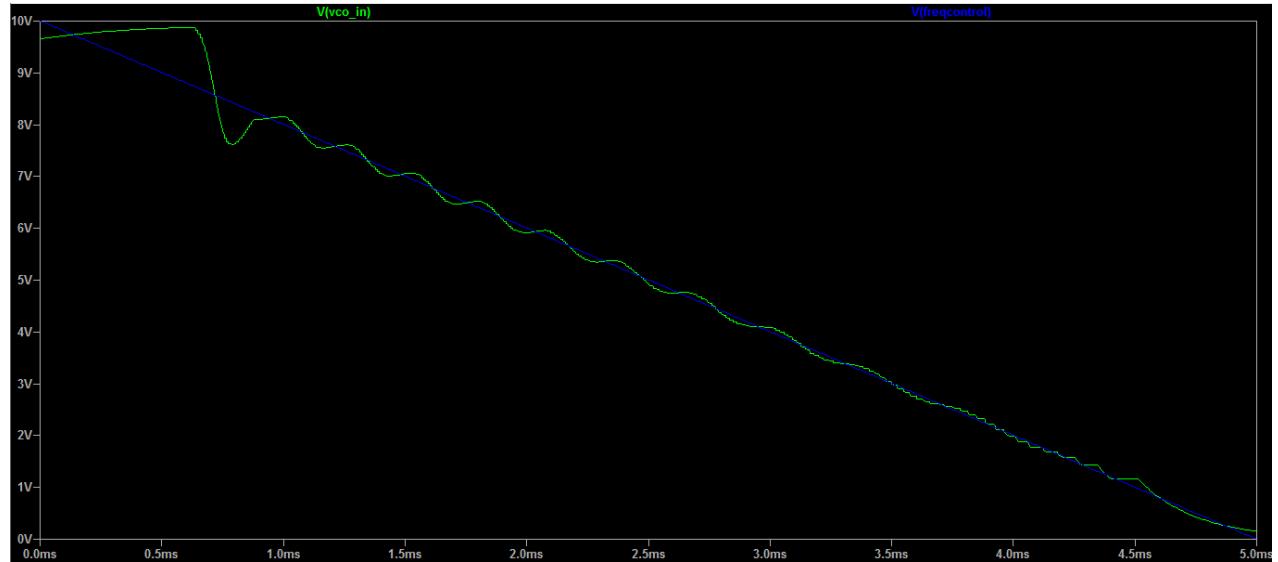


C2=10nF:

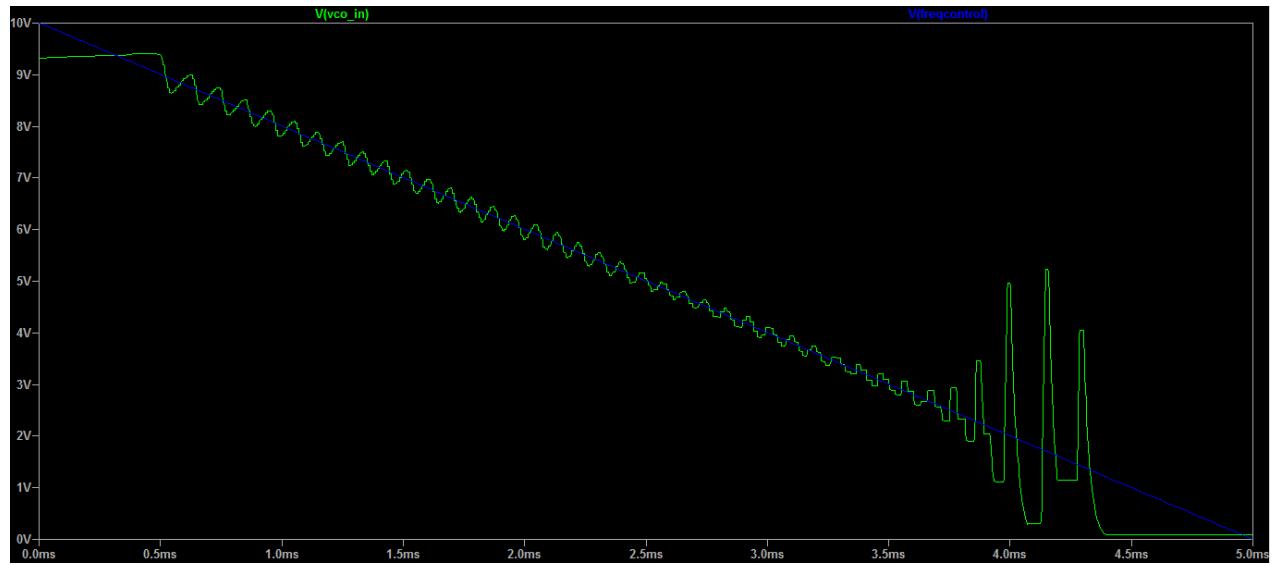


(2)Pc1

C2=100nF:

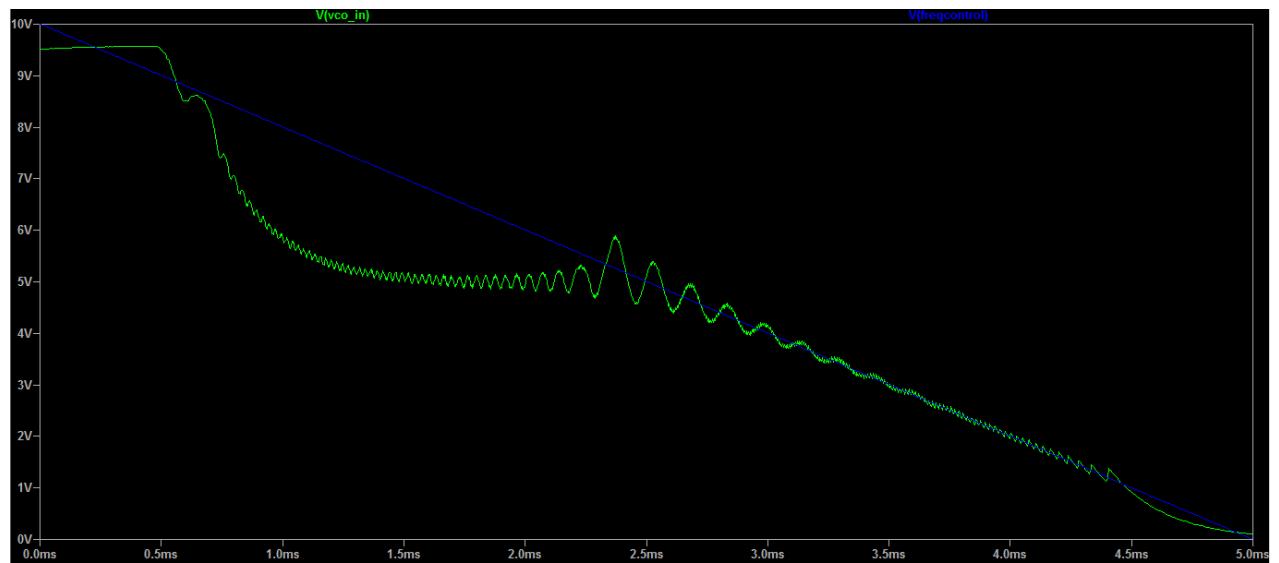

c2=10nF:

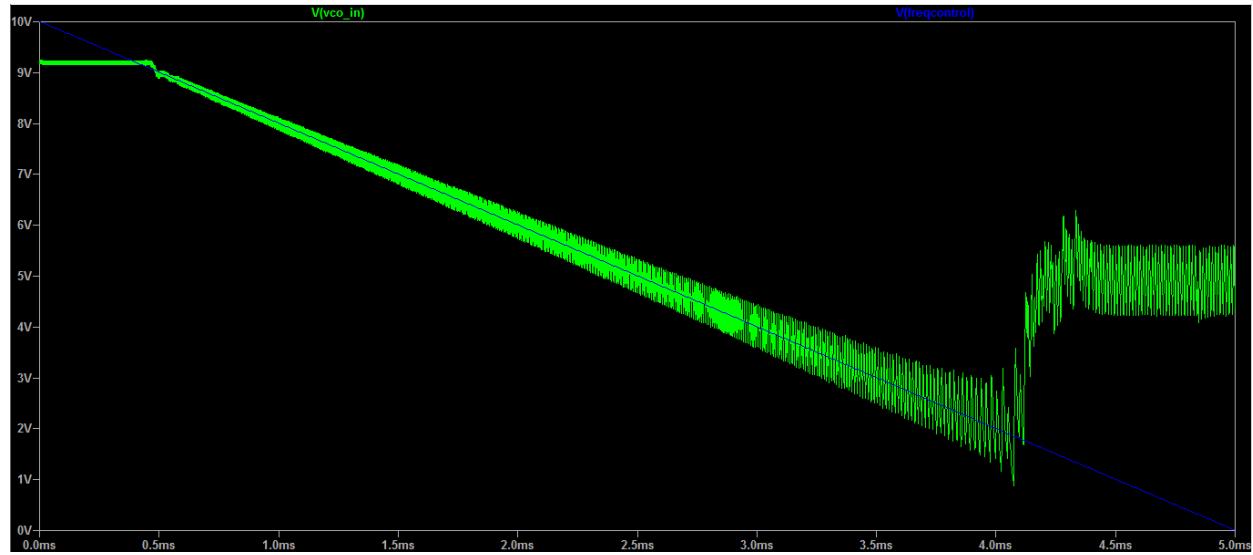

5.


Selon la question 2, on a la relation entre f et v:

$$[0,1]: f=1.95v$$

$$[1,9]: f=19.512v-17.561$$


$$[9,10]: f=1.96v+140.4$$

(1) Croissant ,c2=100nF,pc2

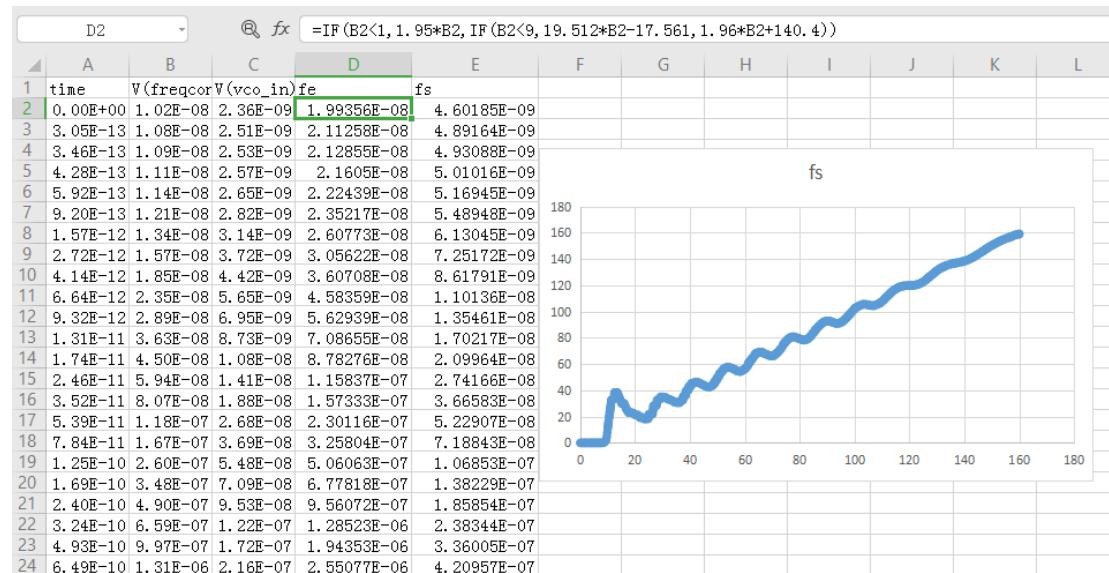

f1=9.6145kHz;f2=159.63kHz

## (2) Decroissant ,c2=100nF,pc2

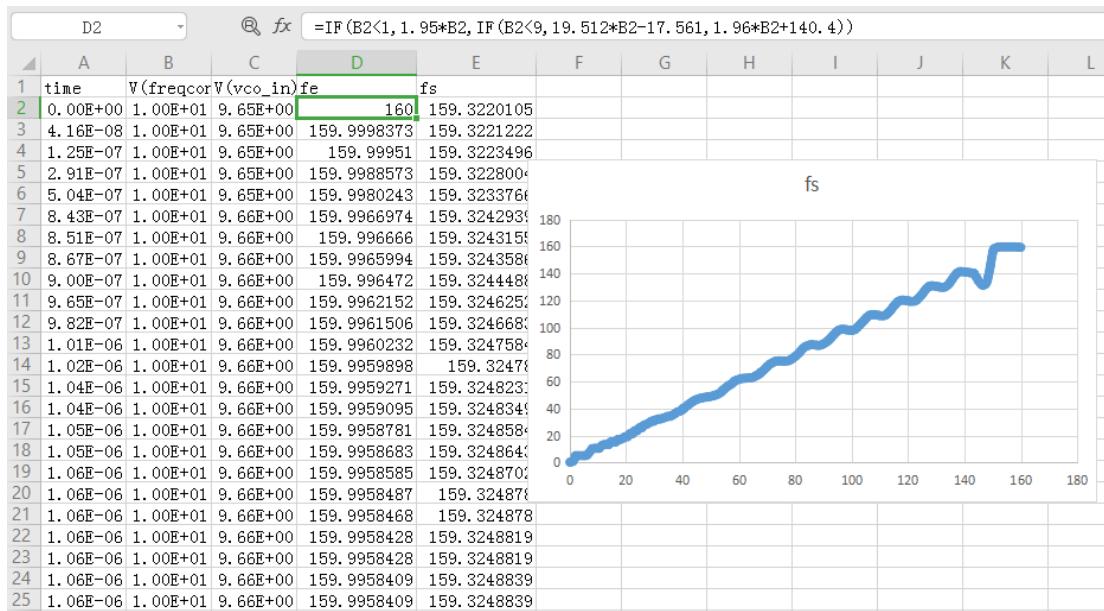


f1=0kHz;f2=149.96kHz

donc pour pc2 c2=100nF

La plage de capture: 9.61-149.96kHz


La plage de verrouillage: 0-159.63kHz

## (3) pc2,C2=10,croissant

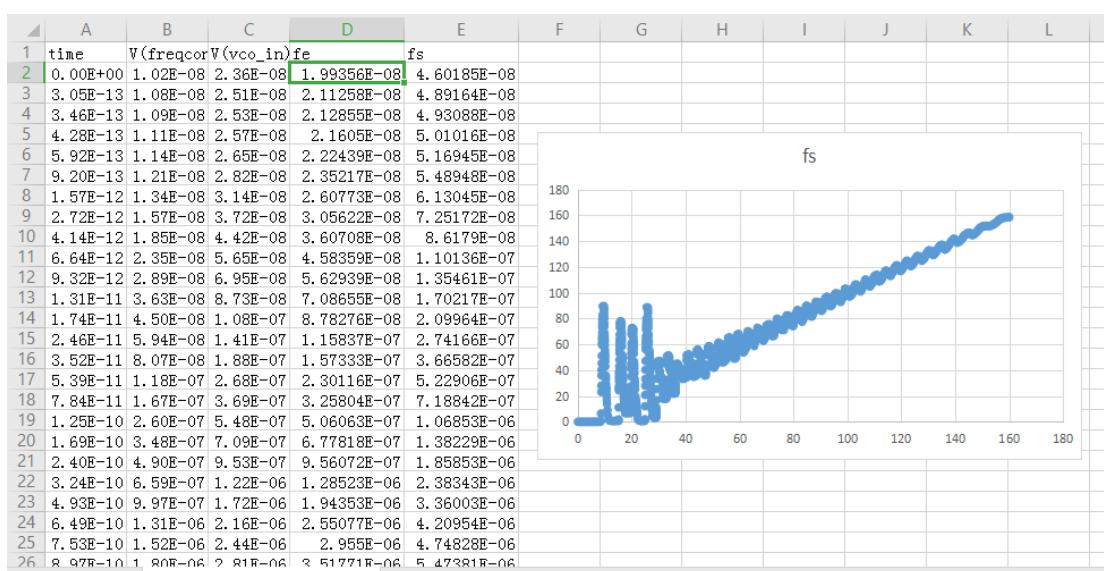


f1=13.90khz;f2=159.63khz.

(4) pc2,C2=10,decroissant

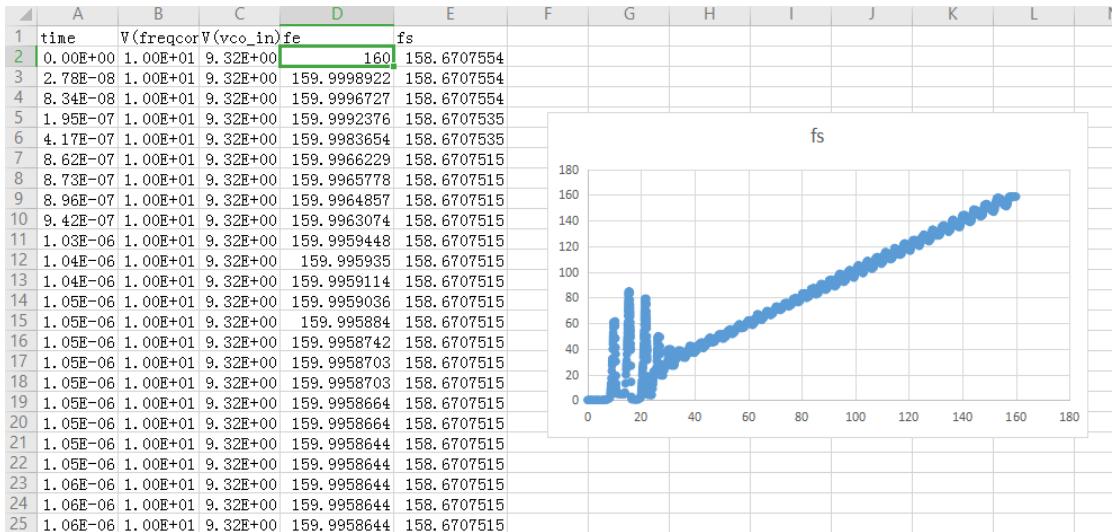


f1=4.96khz;f2=154.16khz

(5)pc1,C2=100nF,croissant

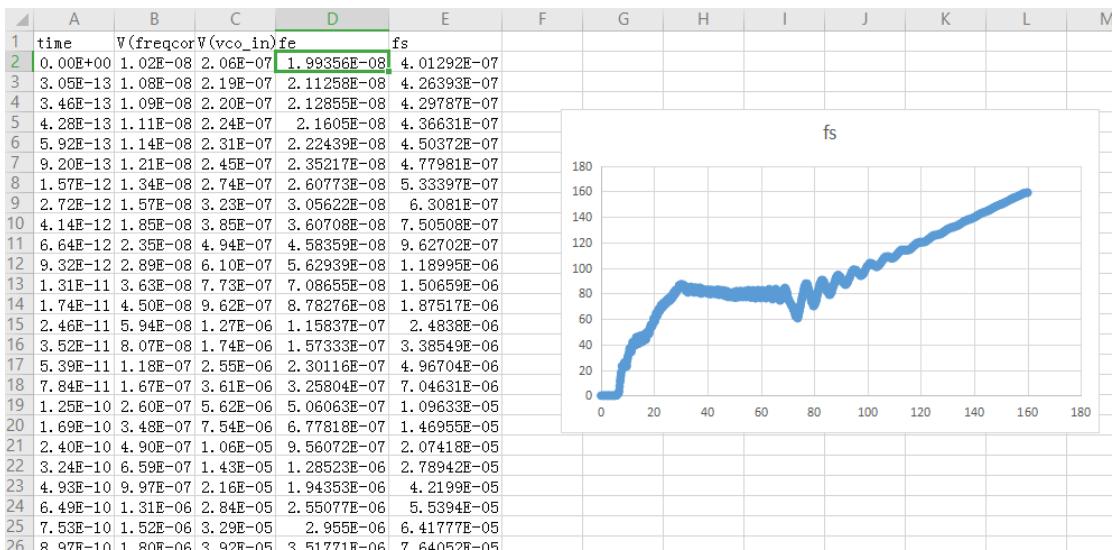

f1=6.81khz,f2=159.63khz.

(6)pc1,C2=100nF,decroissant

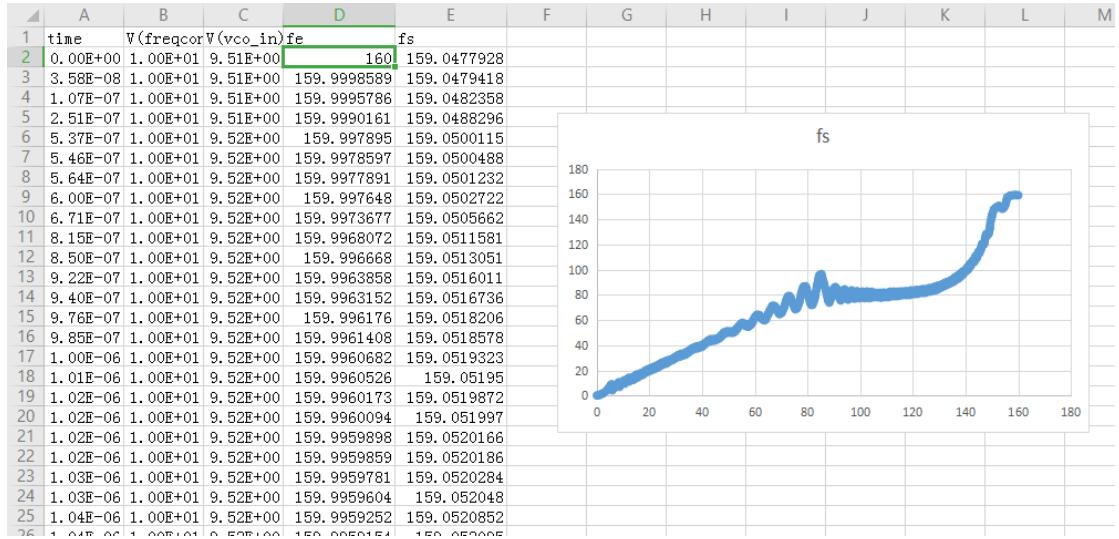


f1=0khz,f2=155.84khz.

La plage de capture:6.81-155.84khz


la plage de verrouillage: 0-159.63khz.

(7)pc1,C2=10nF,croissant

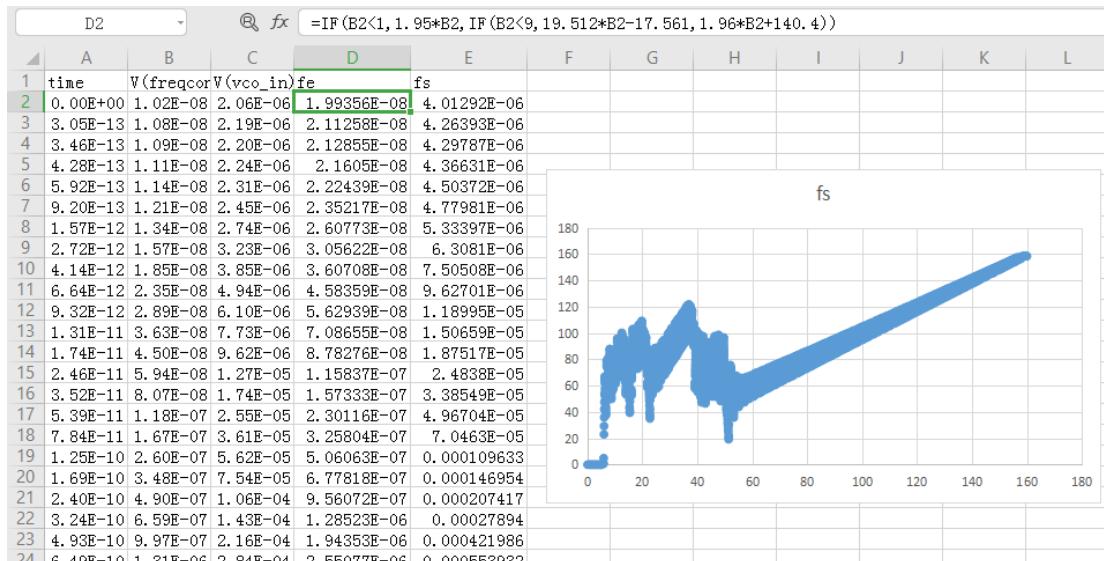

f1=5.83khz,f2=159.63khz.

(8)pc1,C2=10nF,decroissant

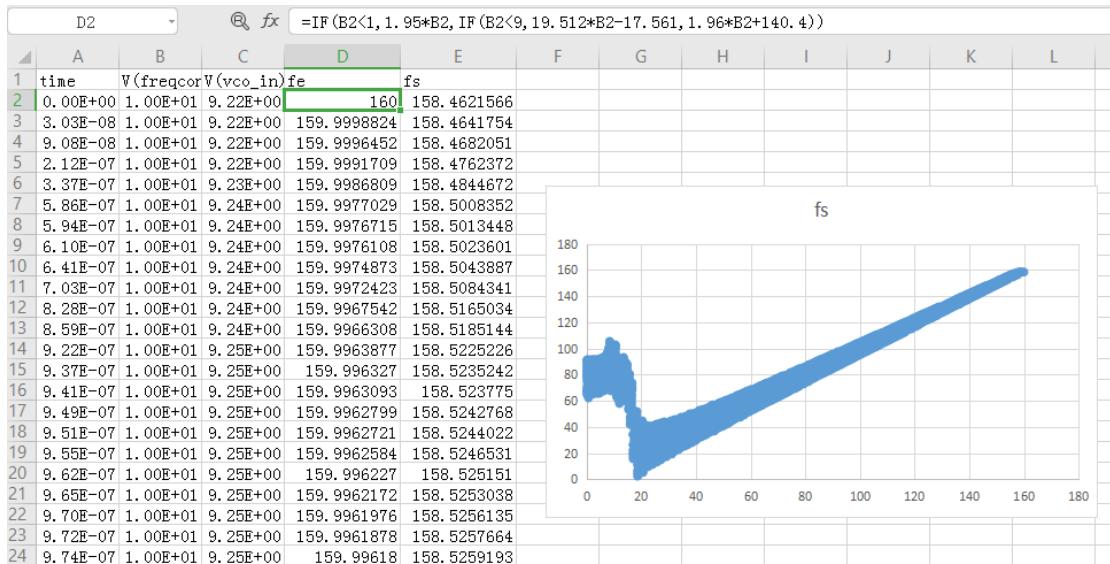


$f_1=0\text{kHz}$ ,  $f_2=155.00\text{kHz}$ .

Donc la plage de capture: 5.83-155.00kHz

plage de verroillage: 0-159.63kHz.


Q3

(1)  $\text{pc1}, \text{C2}=10\text{nF}$

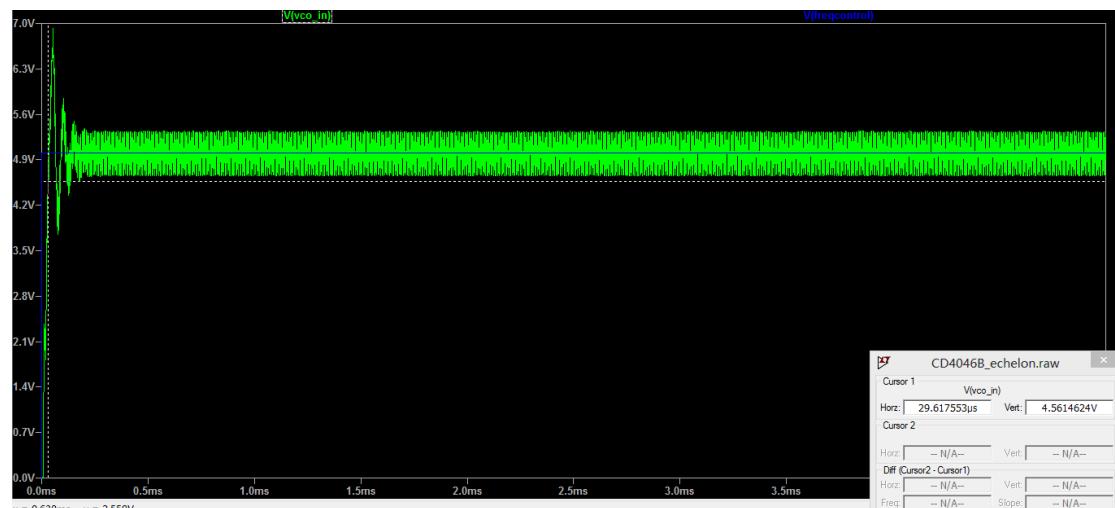


$t=29.62\mu\text{s}$ .

(2)pc1,C2=100nF

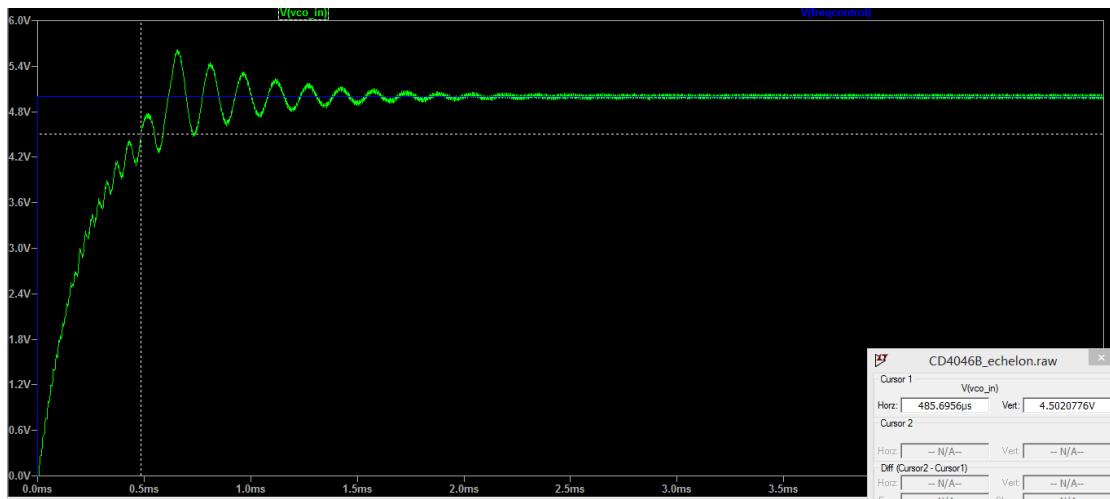


t=485.70us

(3)pc2,C2=10nF

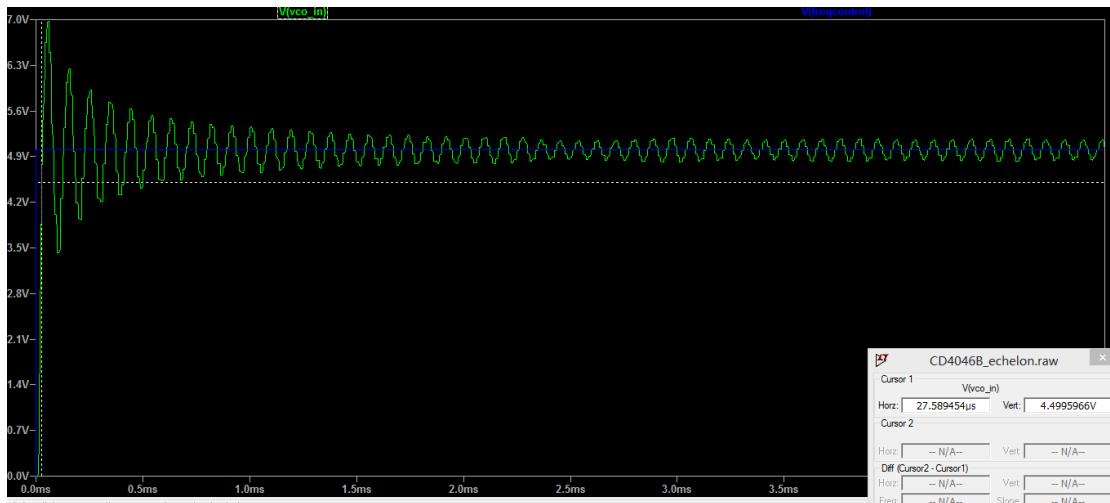

t=27.59us.

(4)pc2,C2=100nF

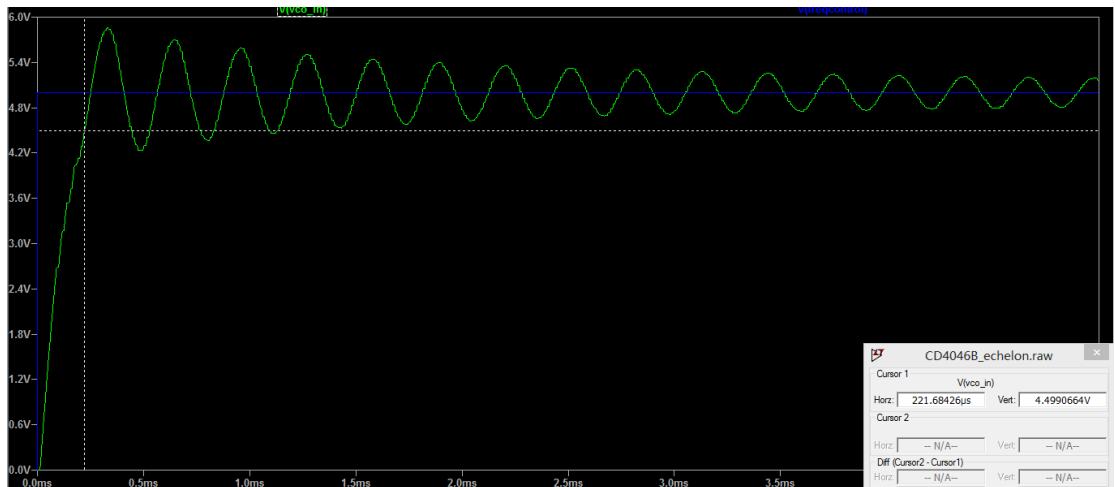

$t=221.68\mu s$ .

On sait que  $t=RC$

Quand  $C_2=100nF$ ,  $R_3=1.8k\Omega$ :

$t=180\mu s$ .

En pratique, pour  $pc1, t=485.70\mu s$ ; pour  $pc2, t=221.68$ .

Quand  $C_2=10nF, R_3=1.8k\Omega$ :

$t=18\mu s$ .

En pratique, pour  $pc1, t=29.62\mu s$ ; pour  $pc2, t=27.59$ .