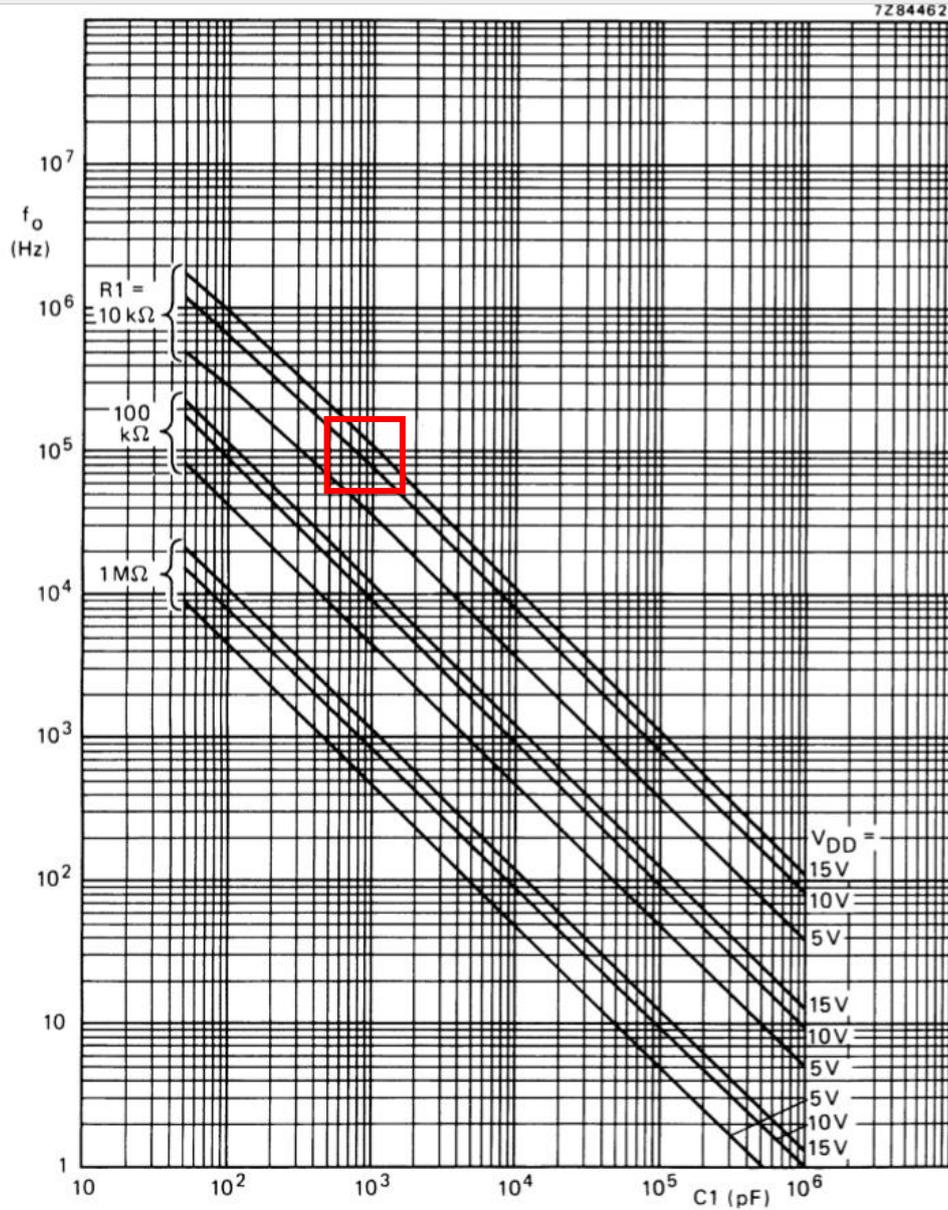


Devoir4

Jules SY1924105

1. Dans figure7, on peut voir que $f_0 \approx 85\text{kHz}$, $f_{\text{max}} = 2f_0 = 170\text{kHz}$, $\text{PLAGE} = 170\text{kHz}$





2.

$V_1 = 0\text{V}$




V1=1V

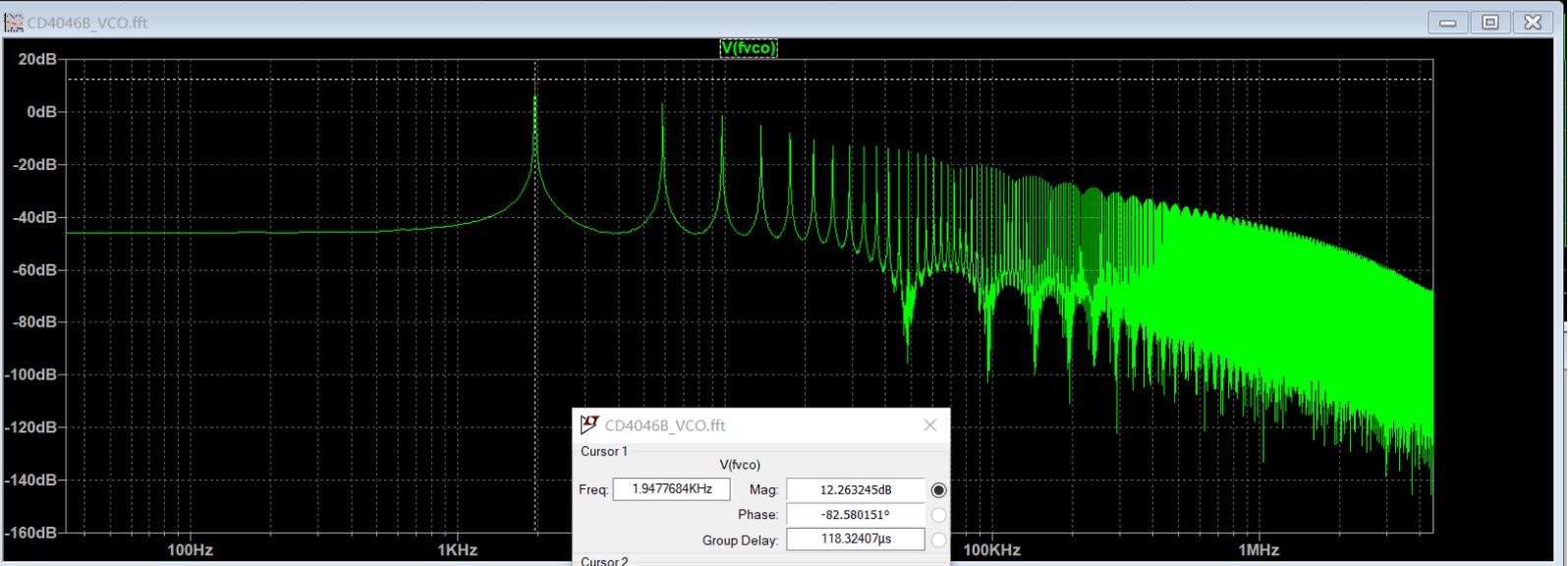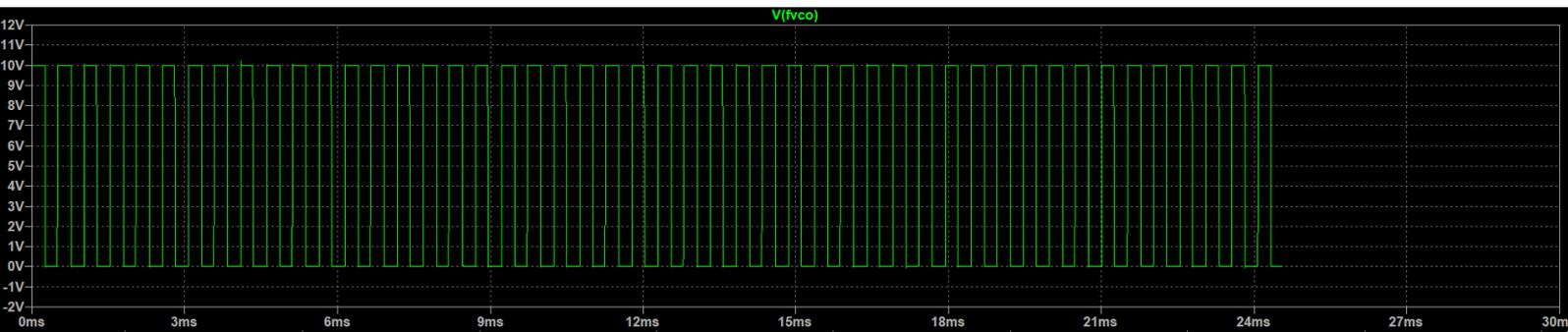


f=1.95kHz, G=12.26dB

V1=2V

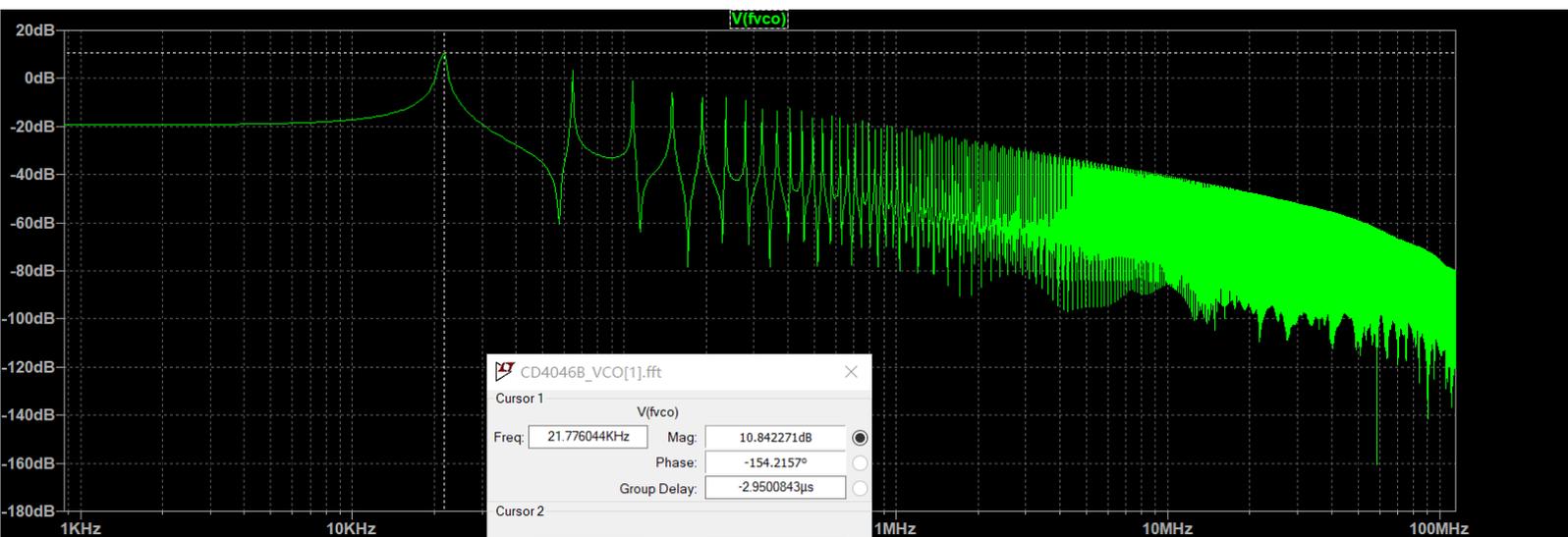


f=21.78kHz, G=10.84dB

V1=3V

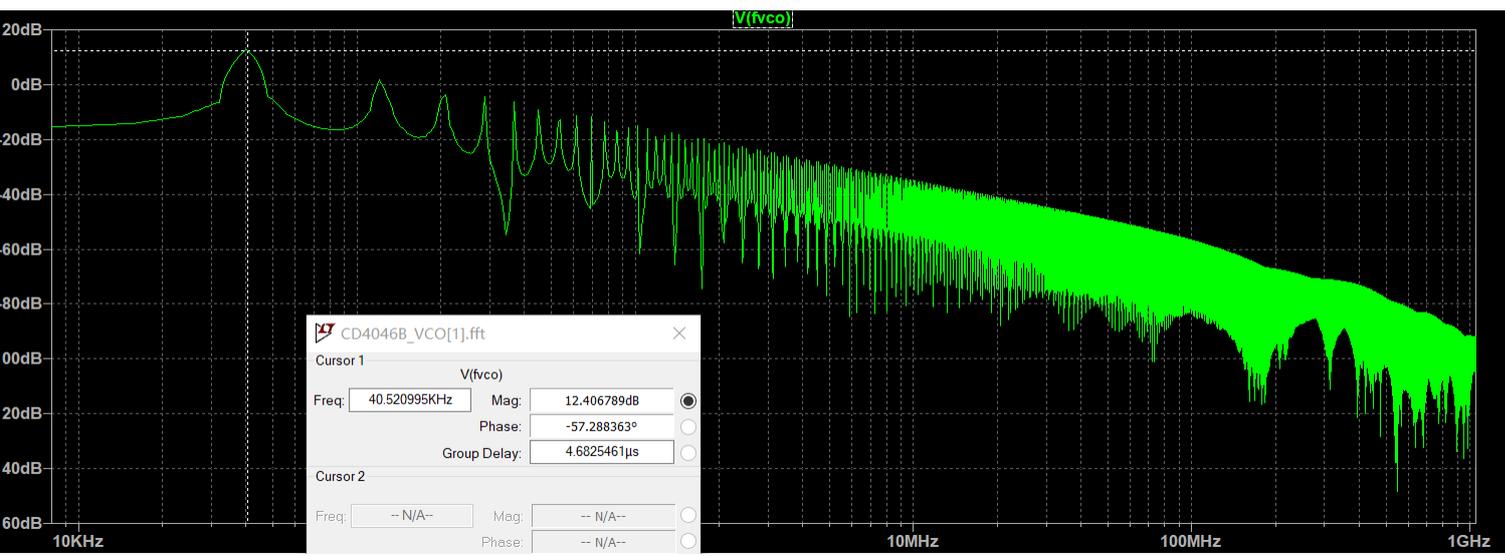


f=40.52kHz, G=12.41dB

V1=4V

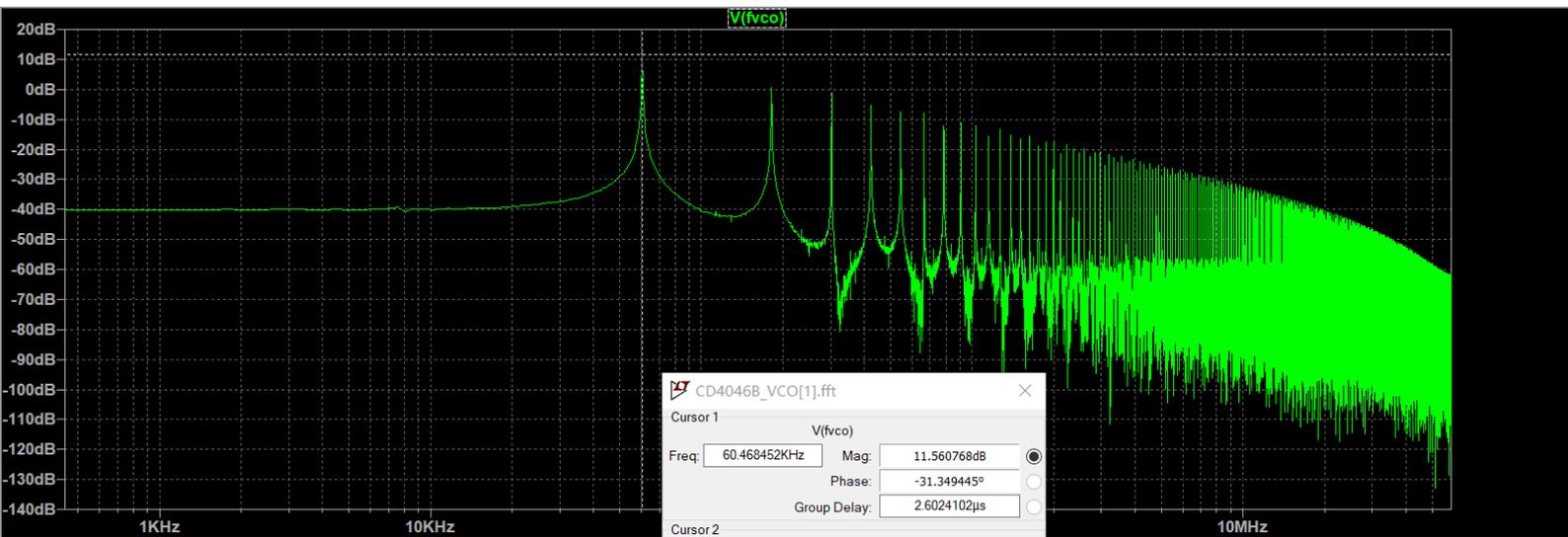


f=60.47kHz, G=11.56dB


V1=5V

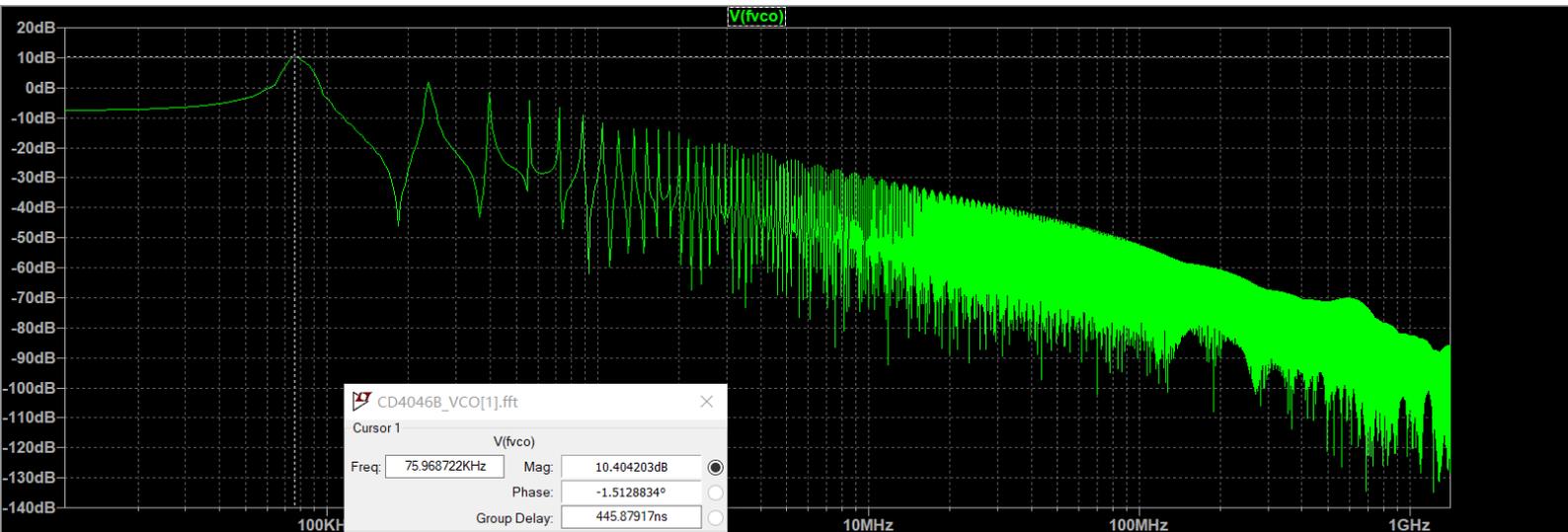


f=75.97kHz, G=10.40dB
V1=6V

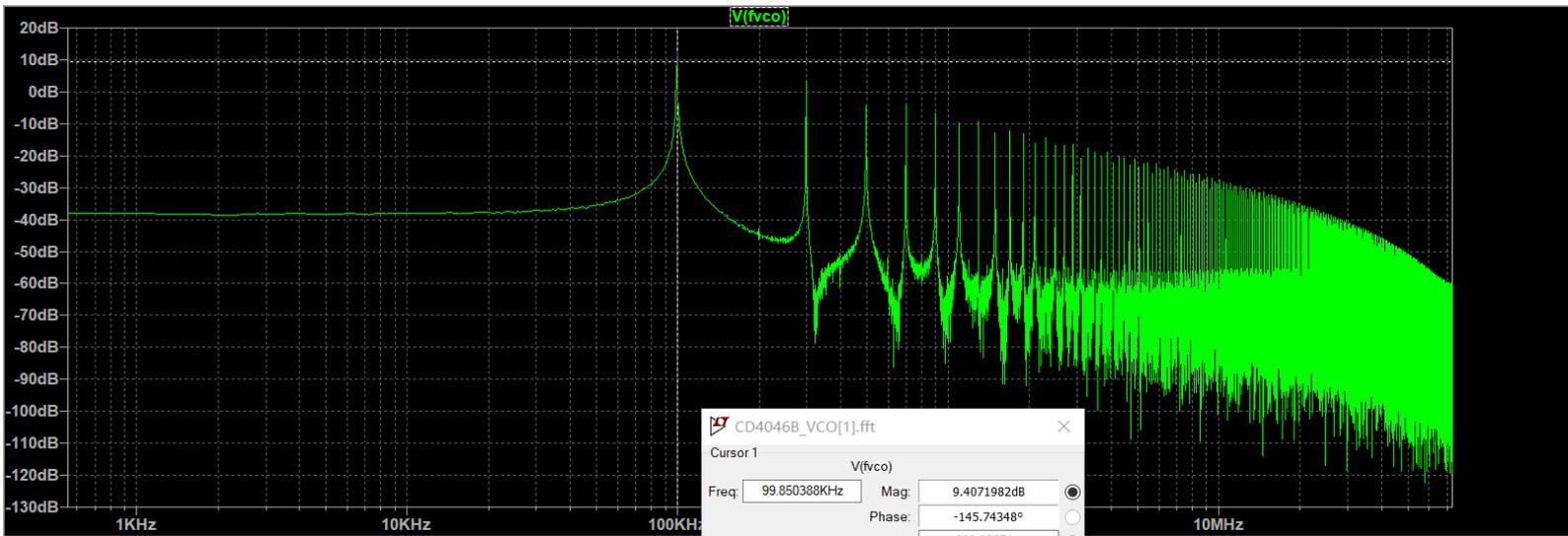


f=99.85kHz, G=9.41dB
V1=7V

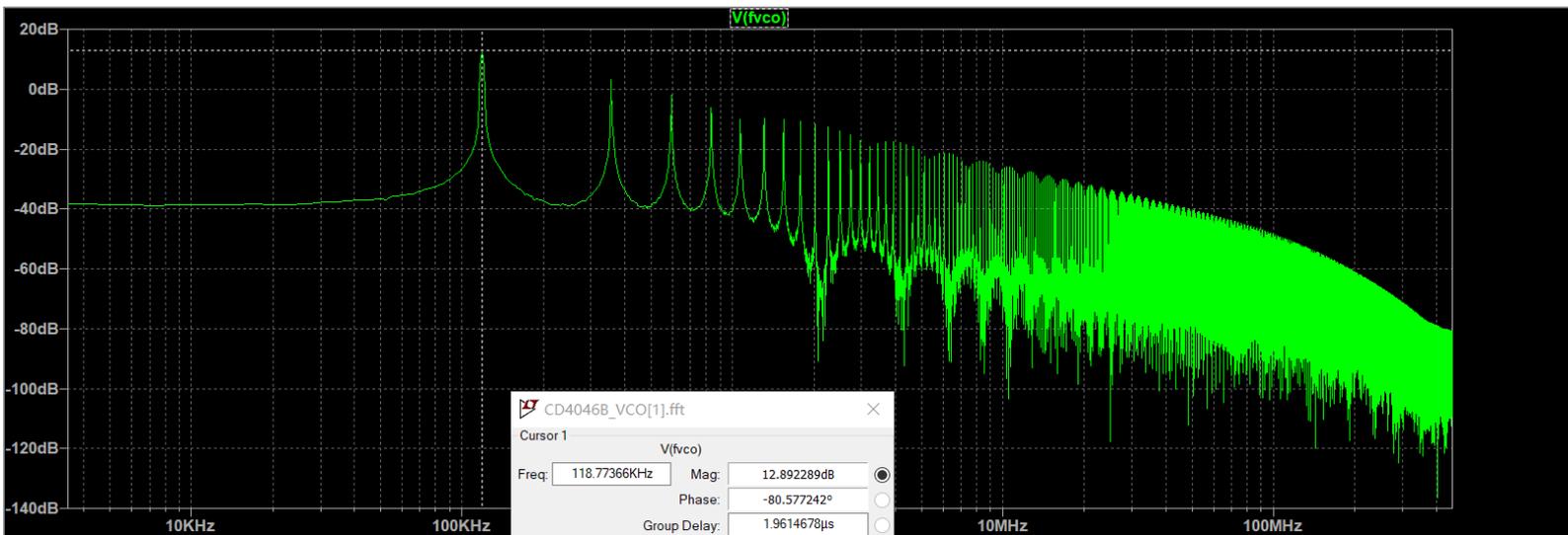


f=118.77kHz, G=12.89dB
V1=8V

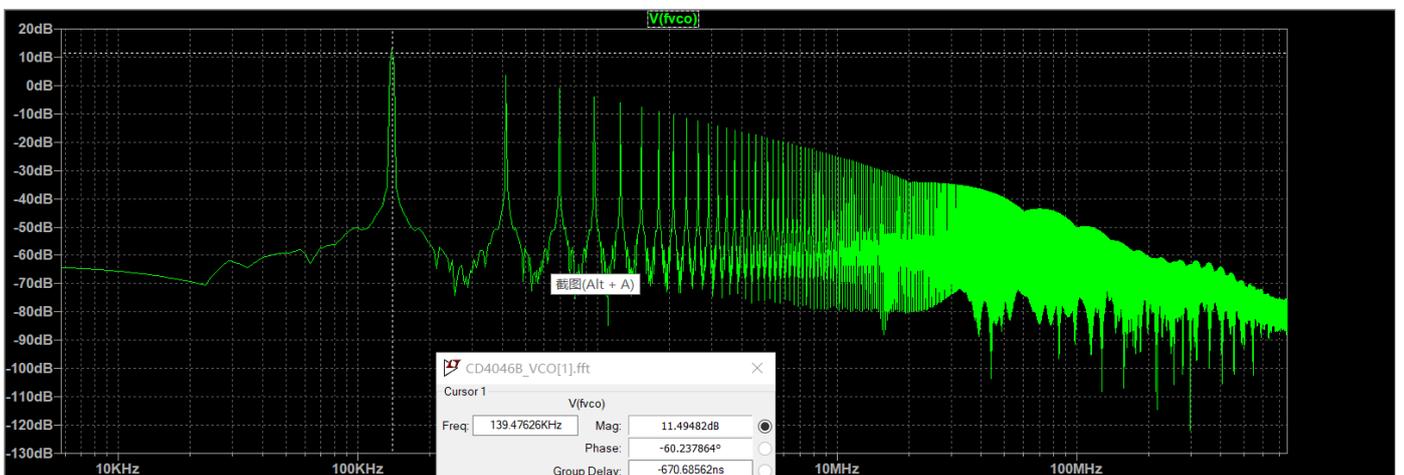

f=139.48kHz, G=11.49dB
V1=9V

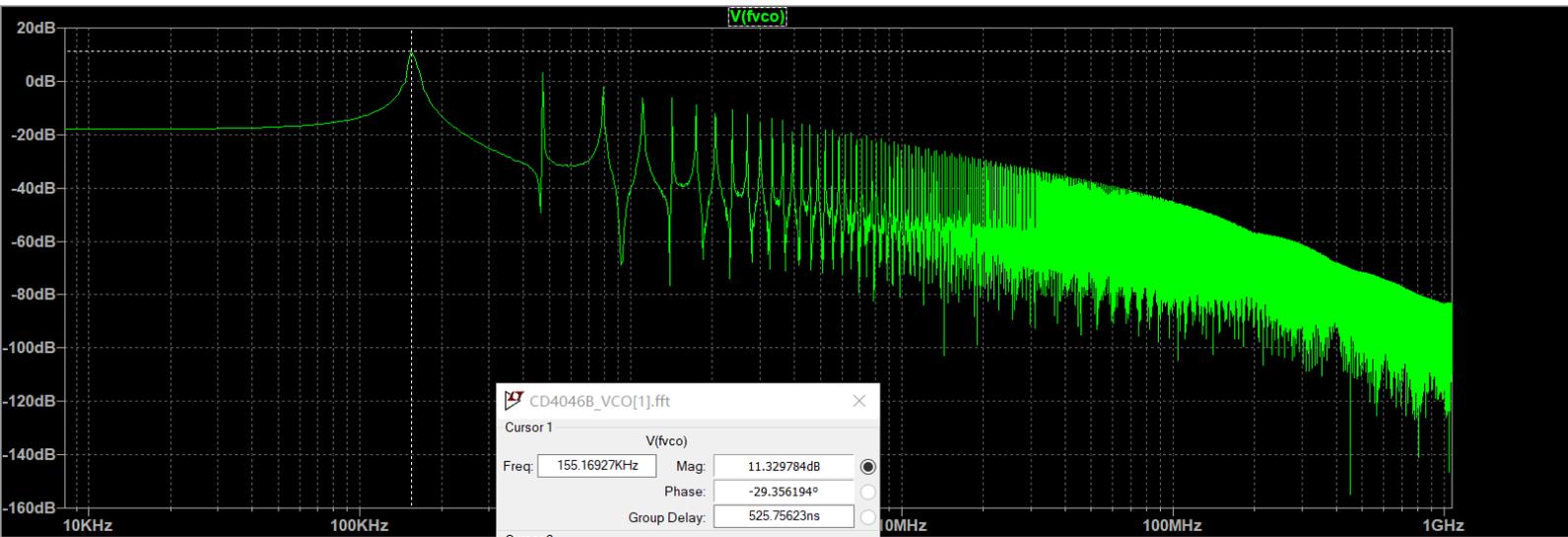


f=155.17kHz, G=11.33dB
V1=10V

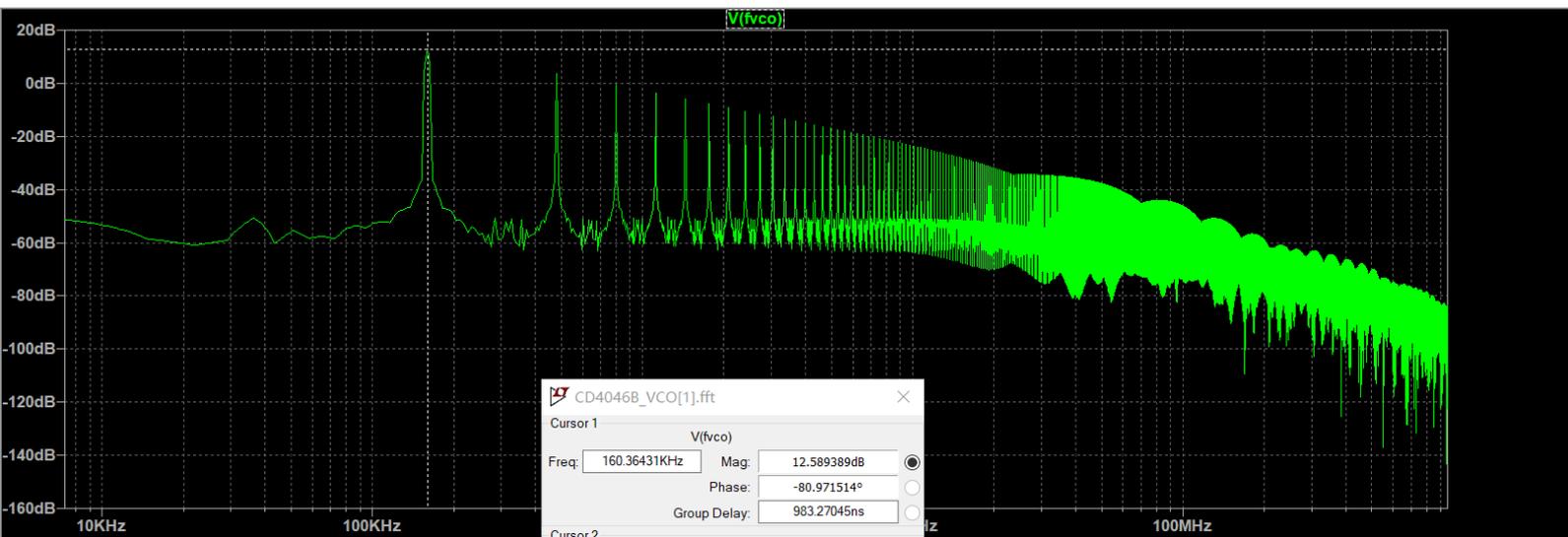

f=160.36kHz, G=12.59dB

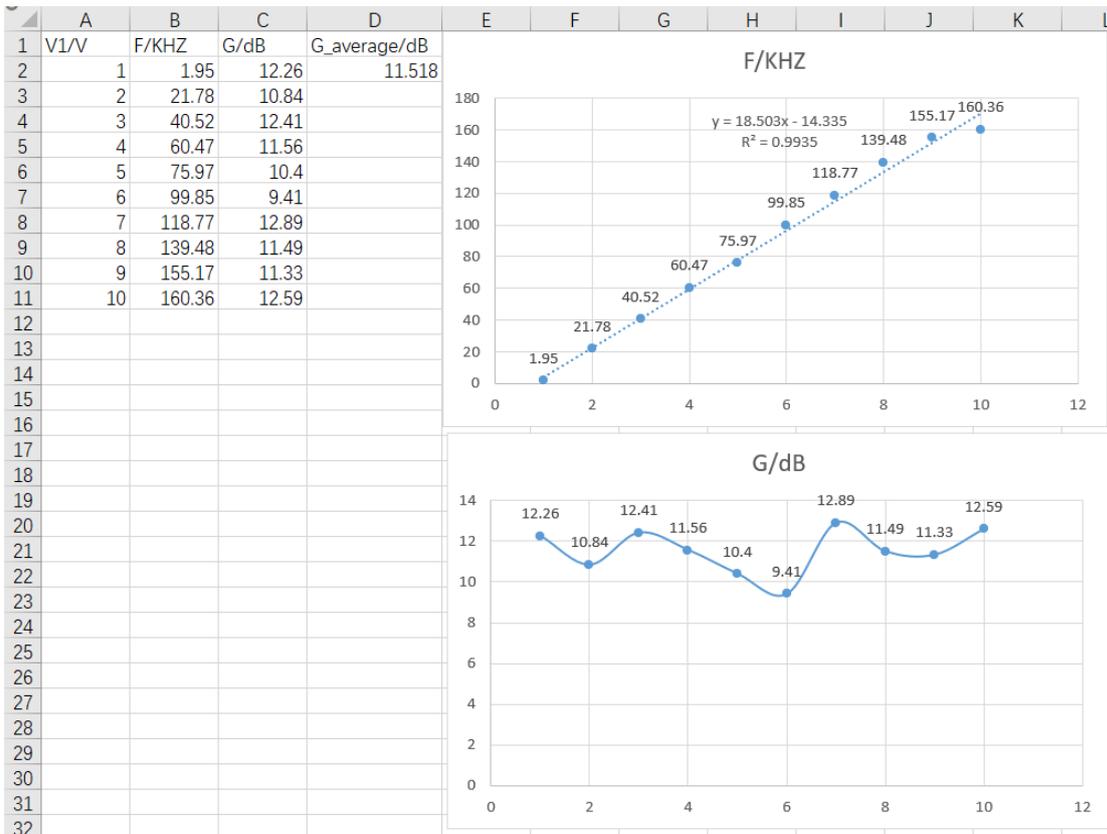On peut voir les résultat dans excel, fréquence f est quasi-linéaire, mais quand V1 est dans [0,1] ou [9,10], la linéarité est mal, et fmax=160.36kHz qui est le même que le modèle




FMAX=0.160 e6.

3.


1) croissante

1.1) pc2


C2=100nF

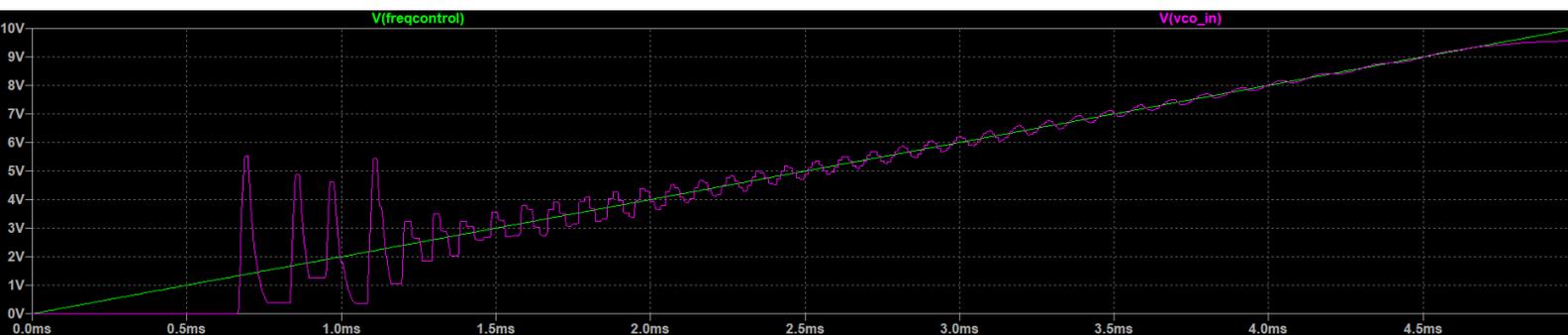

1.2)pc1
C2=100nF

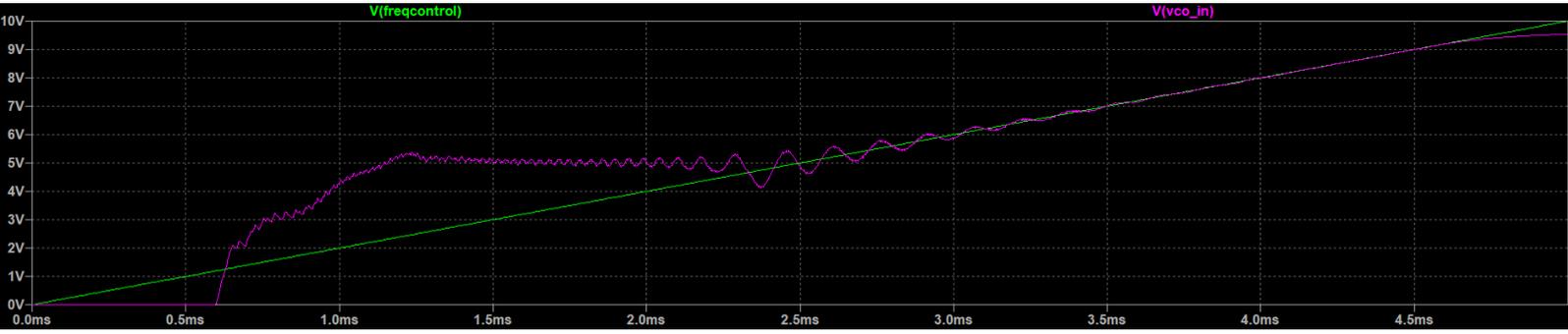


C2=10nF

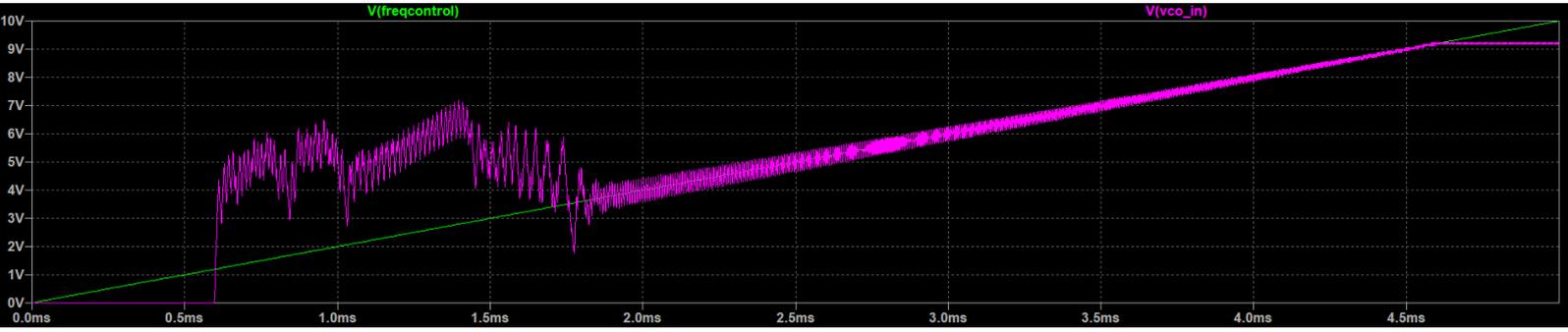


2)decroissante

2.1)pc2
C2=100nF

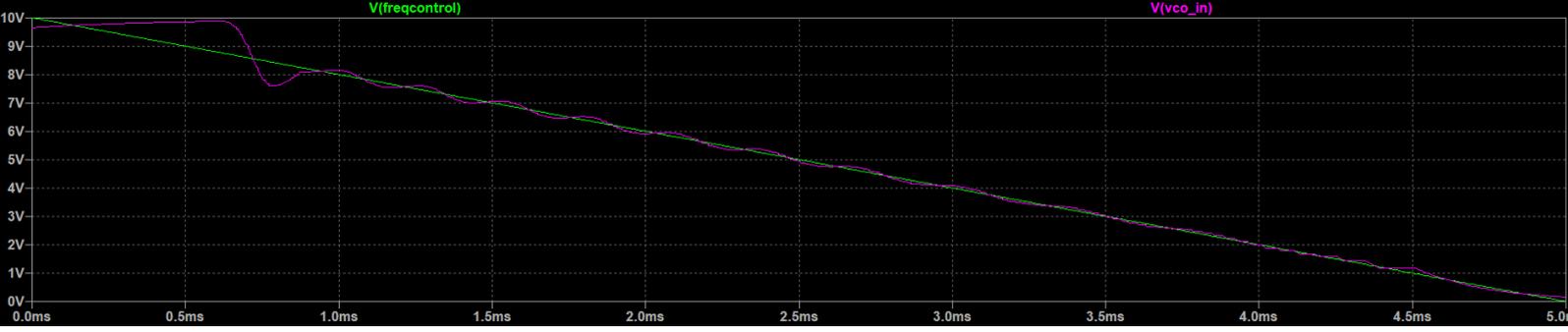


C2=10nF

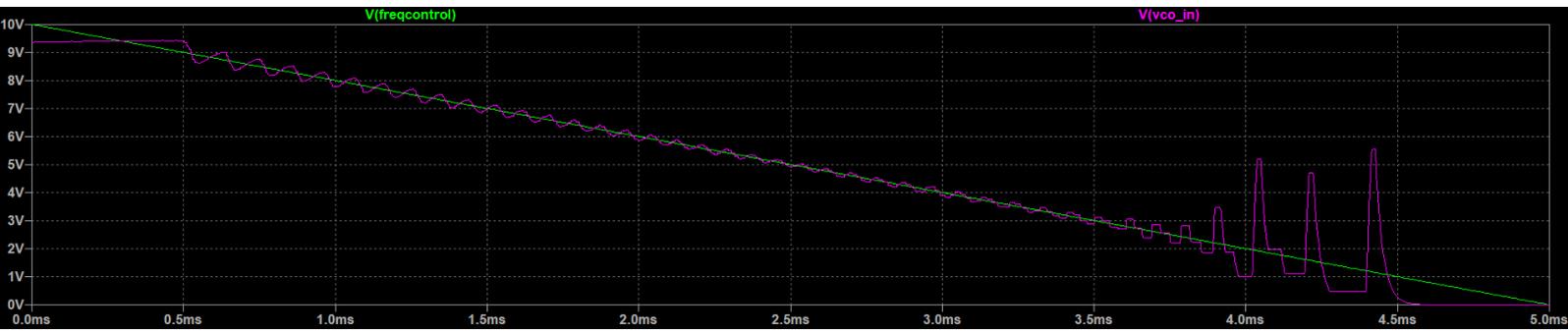


2.2)pc1

C2=100nF

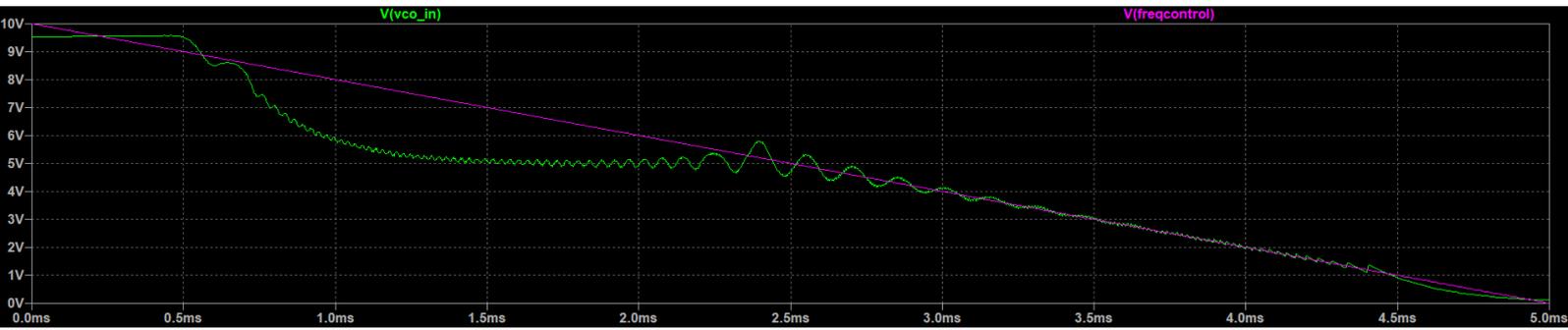

C2=10nF

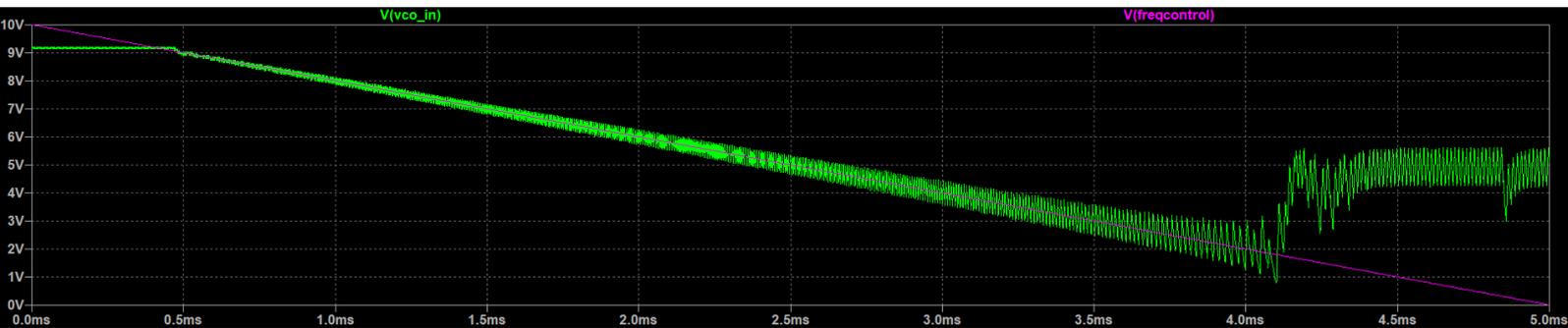

5.


on divise la relation entre f et V dans 3 partie[0,1],[1,9]et[9,10].

$$f = 1.95V$$


$$f = 18.503V - 14.335$$

$$f = 5.19V + 108.46$$

1)pc2 AVEC C2=100nF ET CROISSANTE

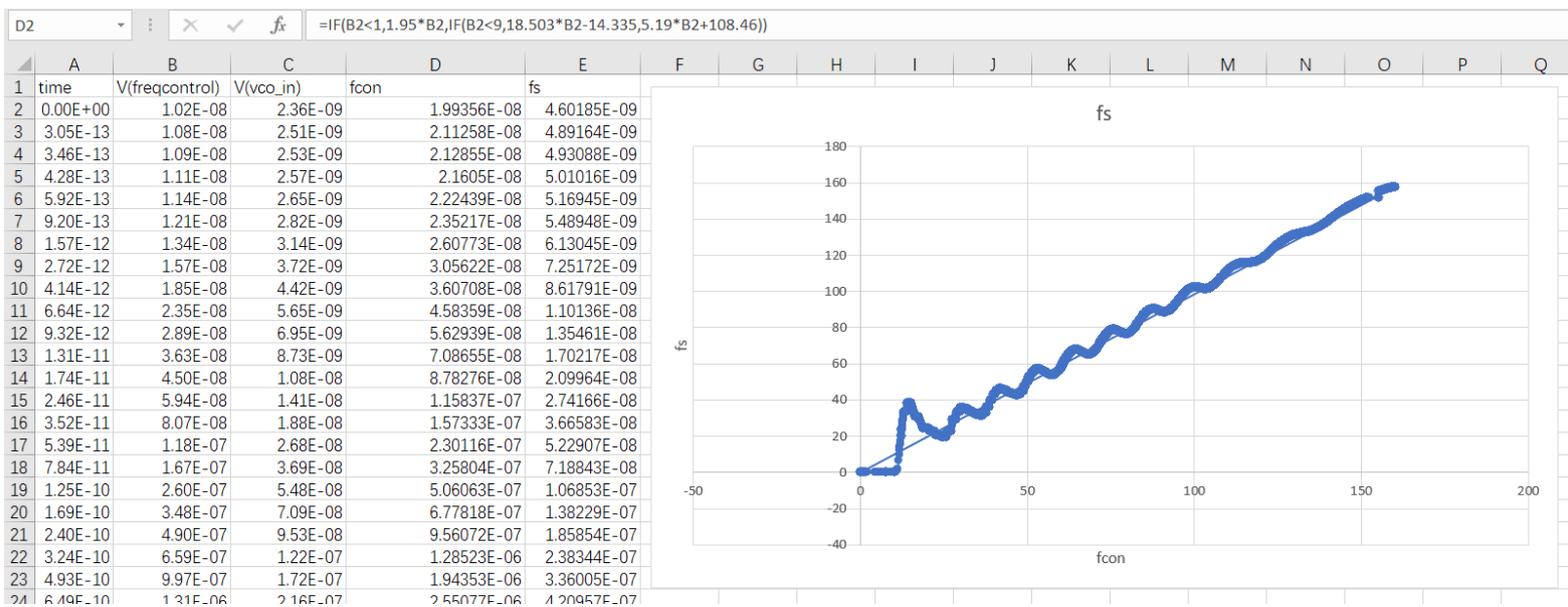

2) pc2 AVEC C2=100nF ET Decroissante

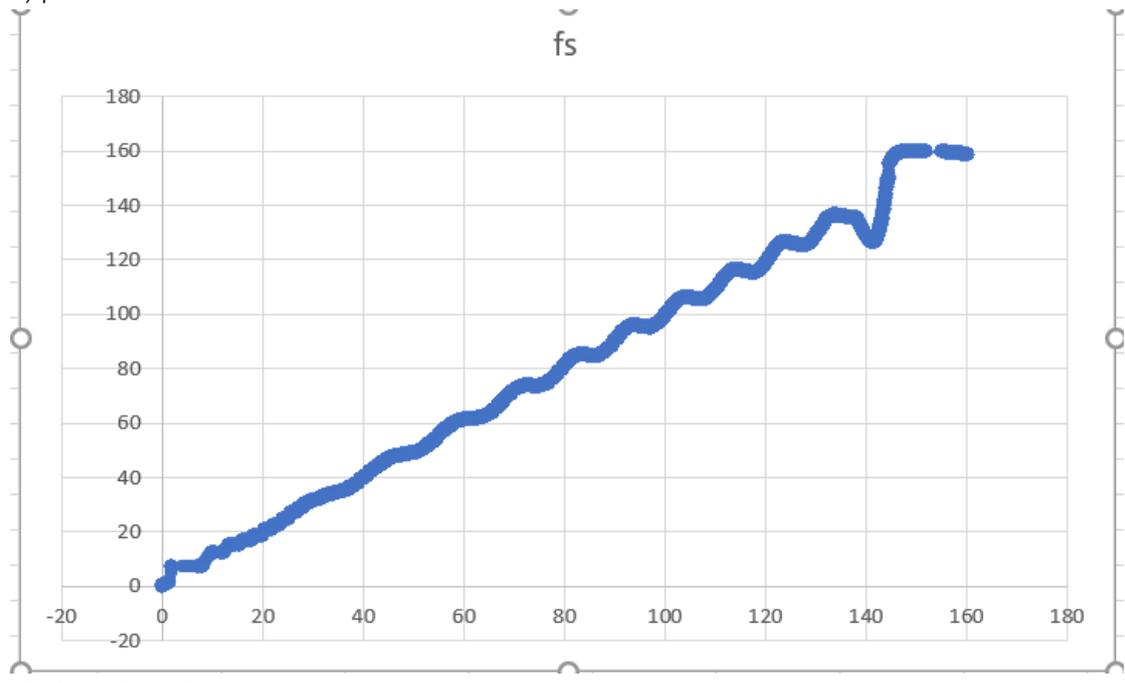


f1=0,f2=145.65kHz

donc pour pc2 C2=100nF

La plage de capture :10.77-145.65kHz


La plage de verrouillage :0-160.34kHz

3) pc2 AVEC C2=10nF ET CROISSANTE

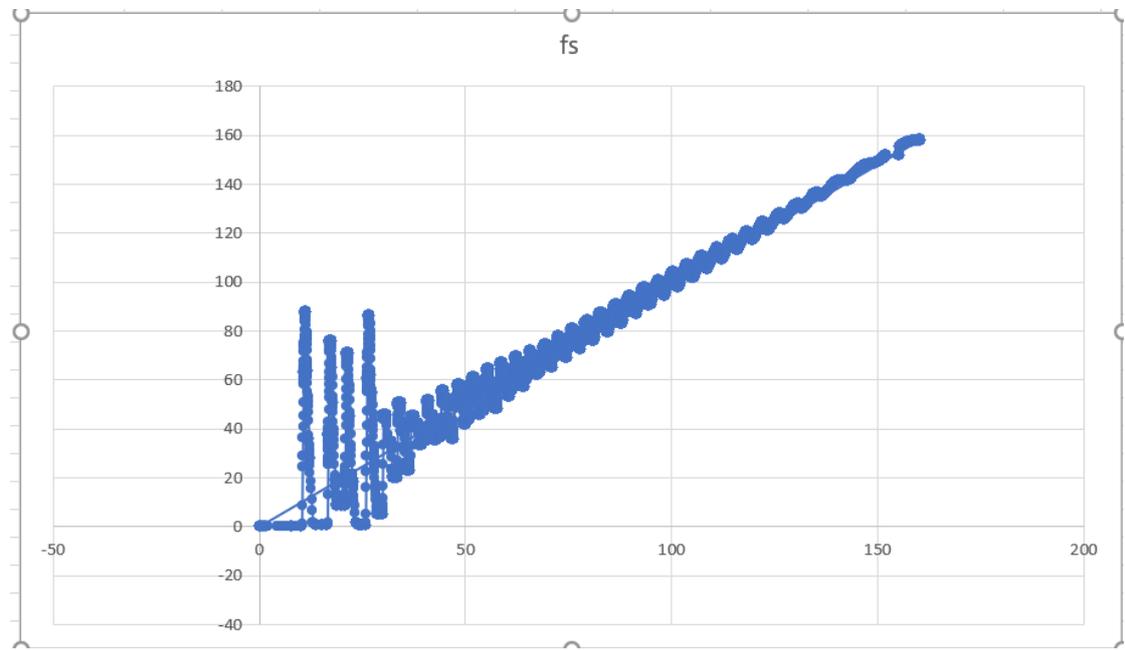

f1=13.31kHz,f2=160kHz

3) pc2 AVEC C2=10nF ET DECROISSANTE

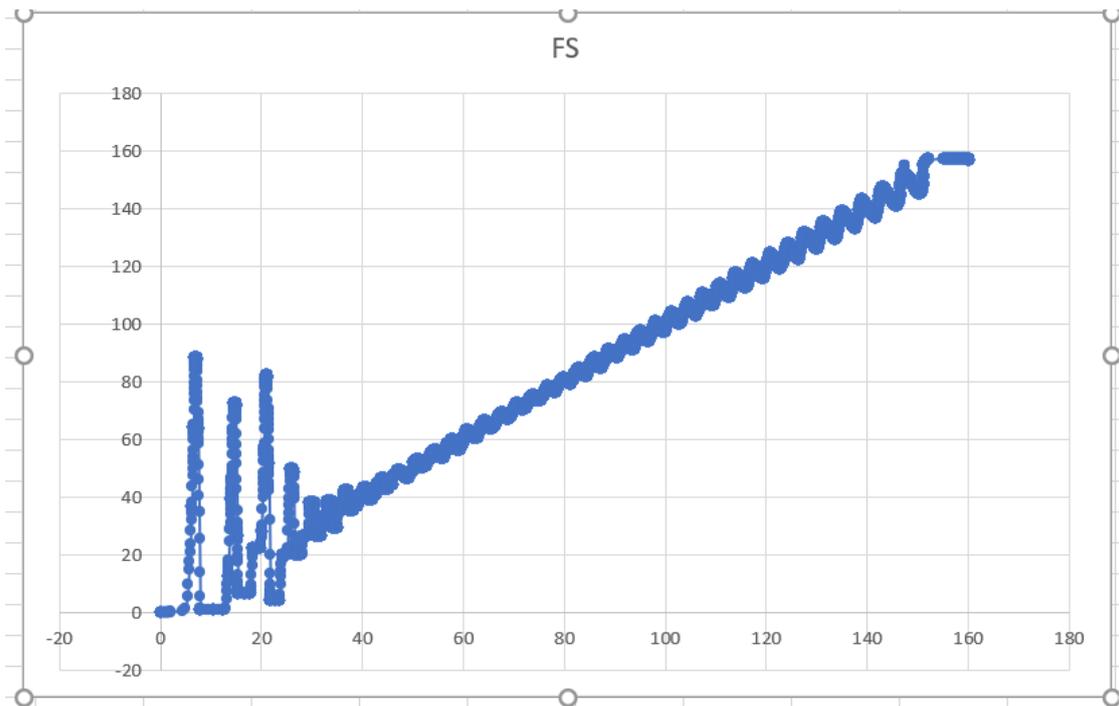


$f_1=4.35\text{kHz}$, $f_2=151.33\text{kHz}$

donc pour pc2 $C_2=10\text{nF}$

La plage de capture :13.31-151.33kHz


La plage de verrouillage :4.35-160kHz

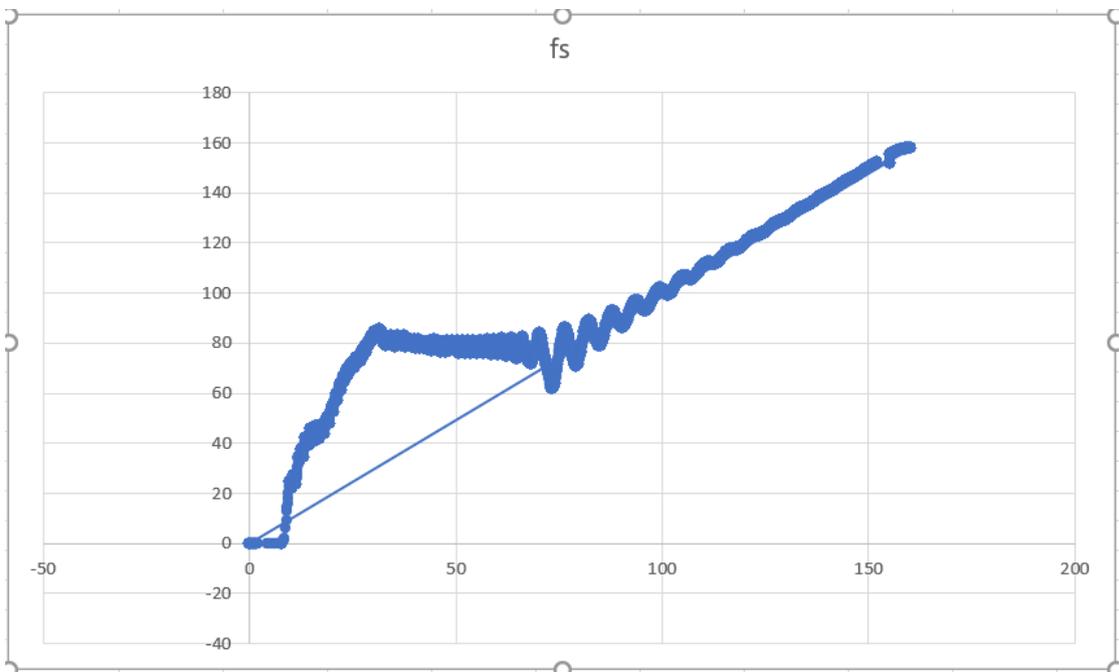5) pc1 AVEC $C_2=100\text{nF}$ ET CROISSANTE



$f_1=8.05\text{kHz}$, $f_2=160\text{kHz}$

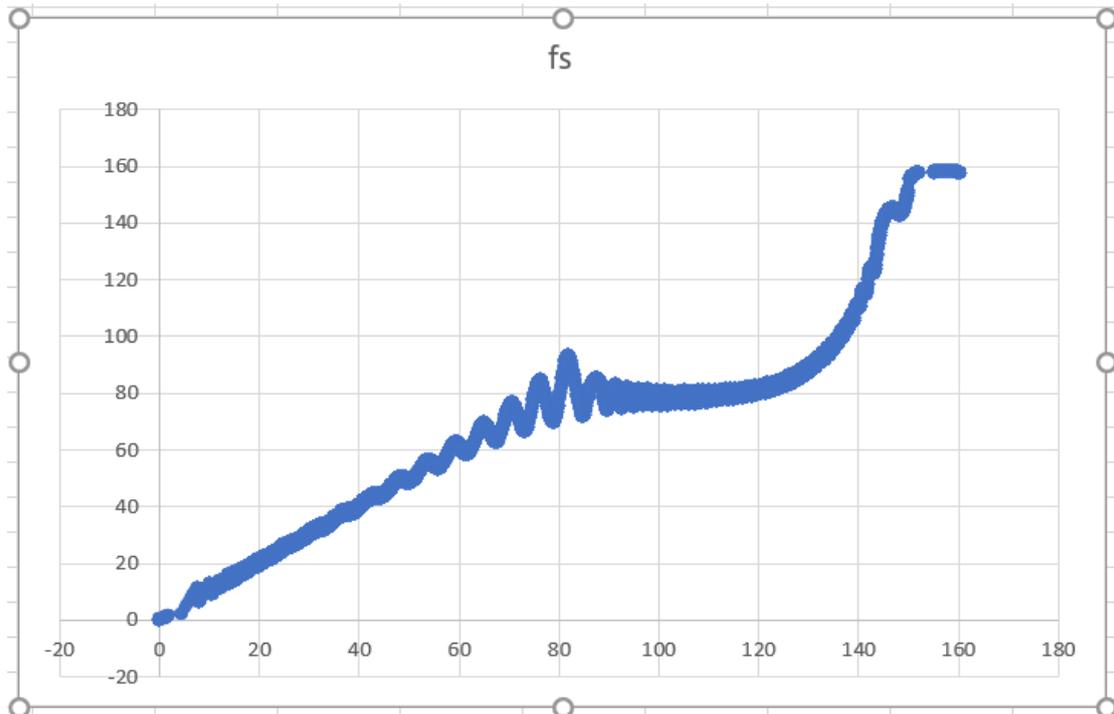6) pc1 AVEC $C_2=100\text{nF}$ ET DECROISSANTE




$f_1=0, f_2=150.29\text{kHz}$

donc pour pc1 $C_2=100\text{nF}$

La plage de capture : $8.05-150.29\text{kHz}$


La plage de verrouillage : $0-160\text{kHz}$

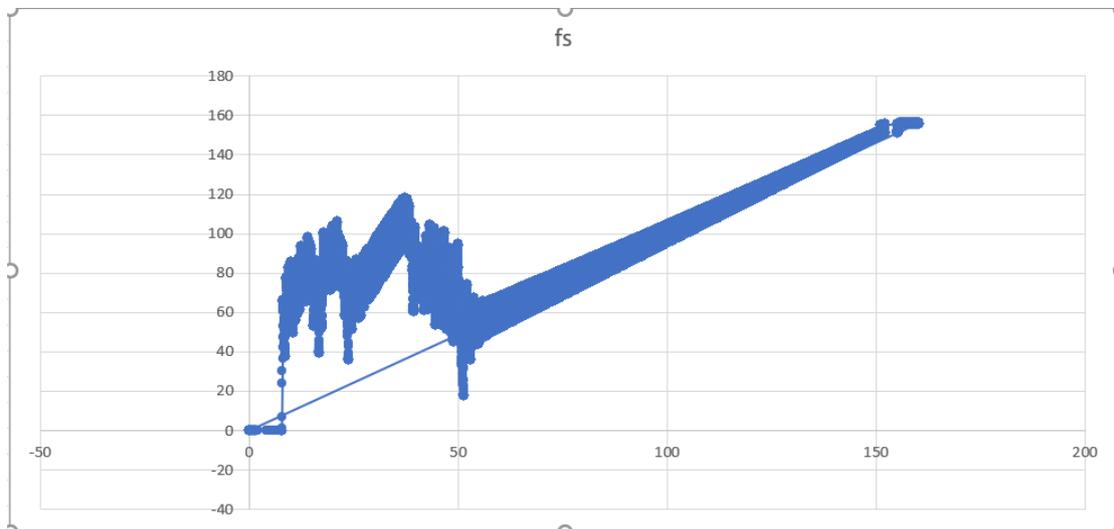7) pc1 AVEC $C_2=10\text{nF}$ ET CROISSANTE




$f_1=7.78\text{kHz}, f_2=157.20\text{kHz}$

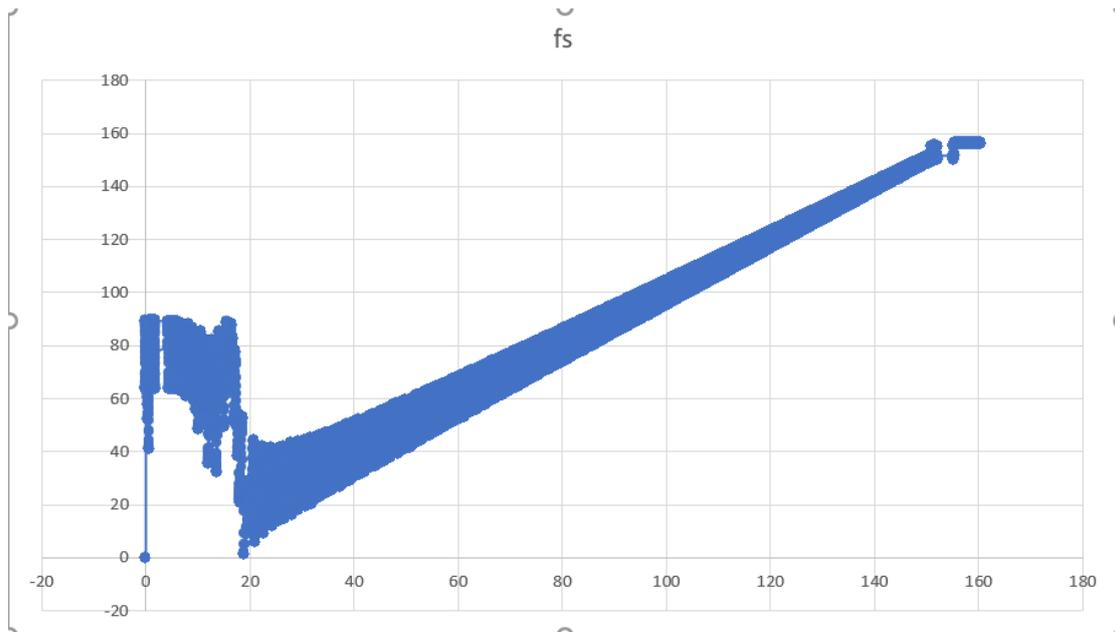
8) pc1 AVEC $C_2=10\text{nF}$ ET DECROISSANTE



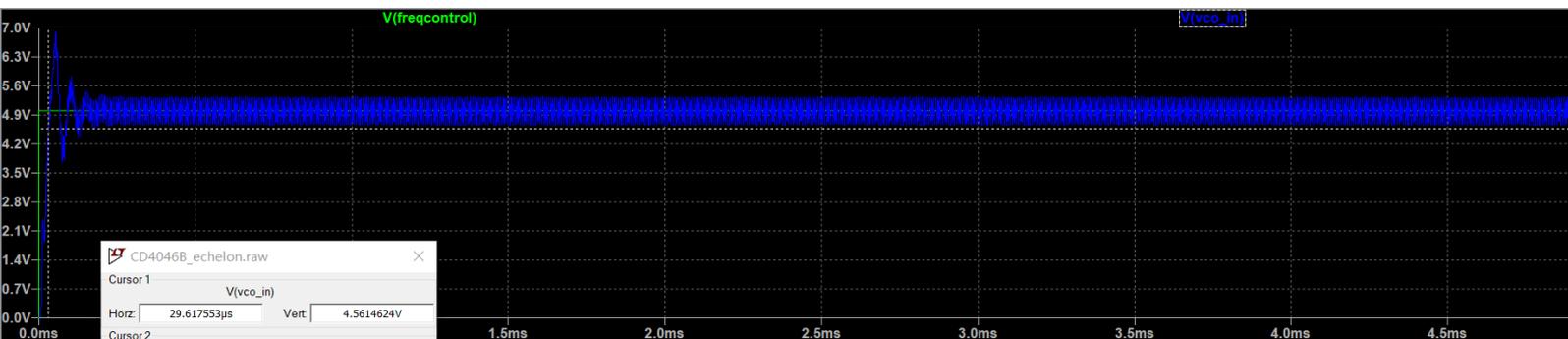$f_1=0, f_2=155.22\text{kHz}$
 donc pour pc1 $C_2=10\text{nF}$
 La plage de capture : $7.78-155.22\text{kHz}$
 La plage de verrouillage : $0-157.20\text{kHz}$
 Q3
 1)pc1, $C_2=10\text{nF}$




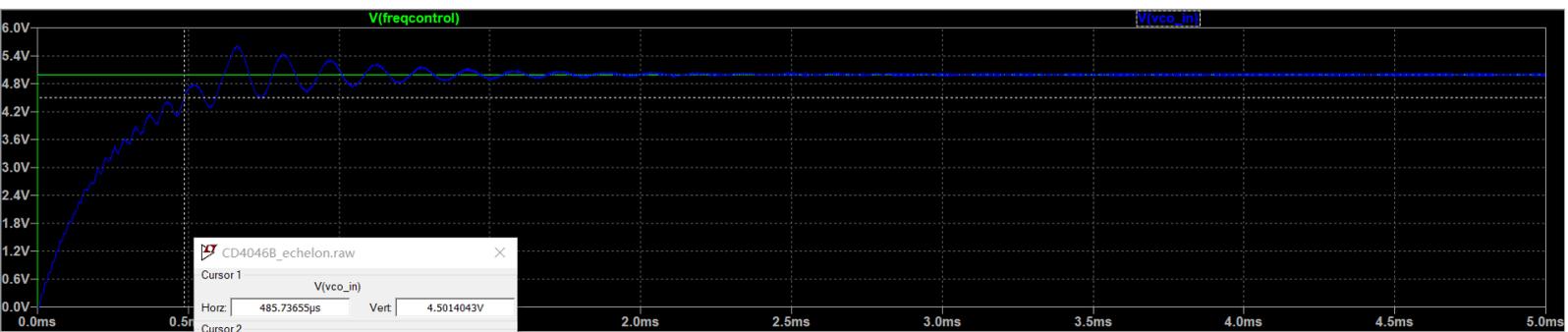$t=29.62\mu\text{s}$
 2)pc1, $C_2=100\text{nF}$




$t=485.74\mu\text{s}$

3) pc2,C2=10nF

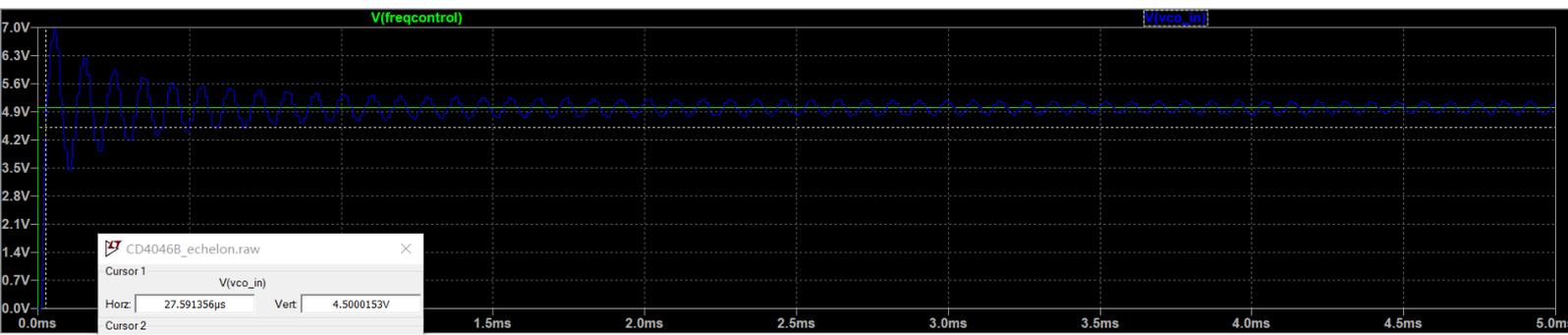

$t = 27.59\mu s$

4)pc2,C2=100nF

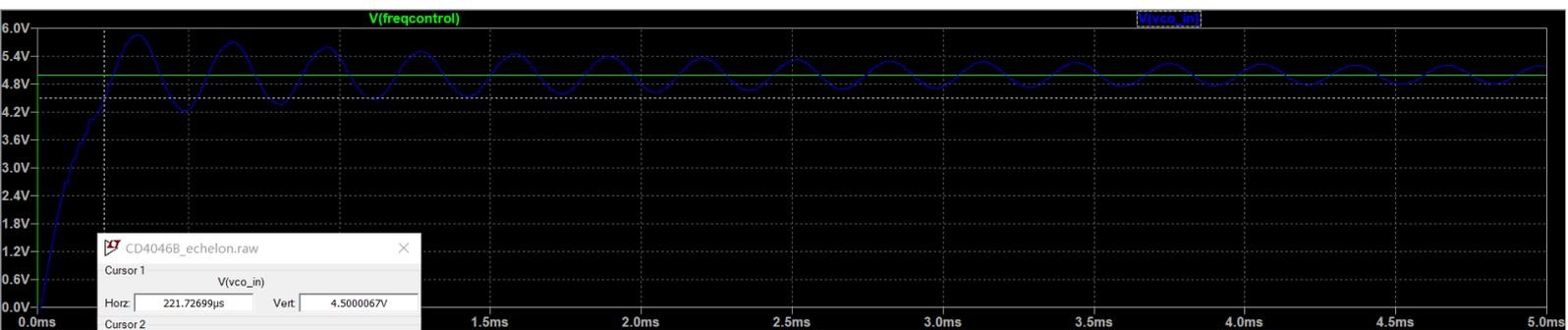

$t = 221.73\mu s$

on sait que

$$\tau = RC$$

1)C2=100nF,R3=1.8k Ω

$$\tau = 180\mu s$$

En fait, pour pc1, $\tau = 485.74\mu s$,pour pc2, $\tau = 221.73\mu s$

2) C2=10nF,R3=1.8k Ω

$$\tau = 18\mu s$$

En fait, pour pc1, $\tau = 29.62\mu s$,pour pc2, $\tau = 27.59\mu s$