
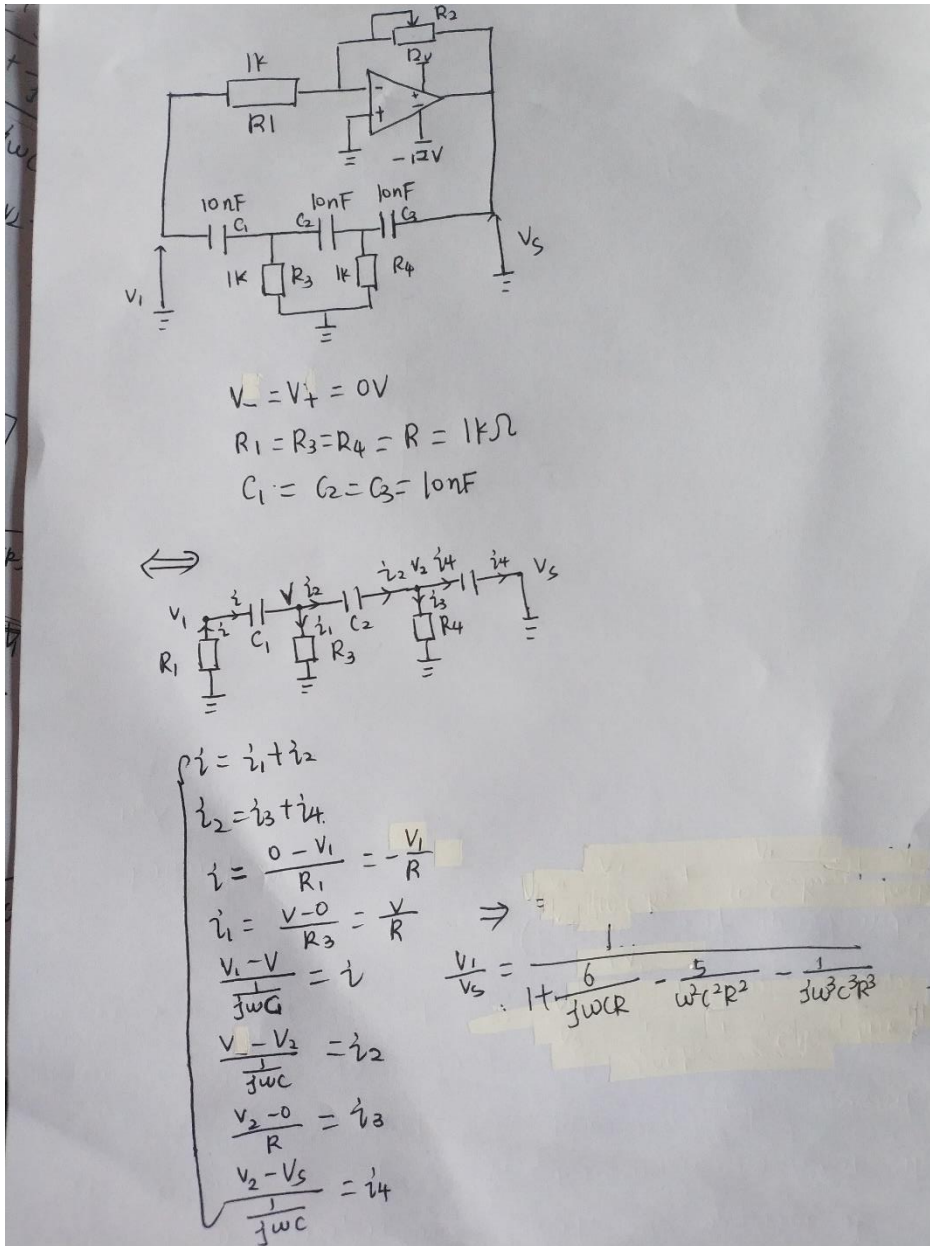


# Oscillateur à déphaseur RC


1.

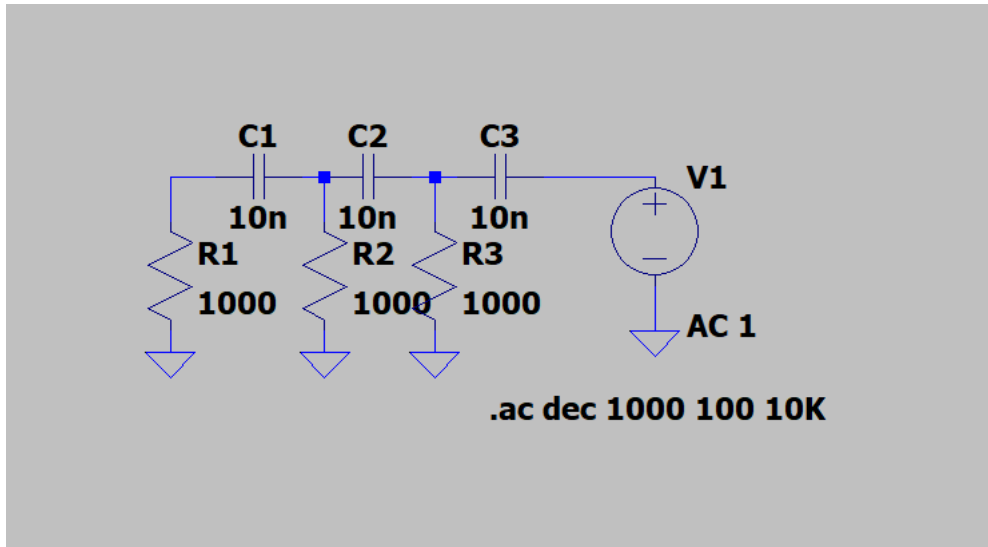

2. Le circuit :



Le résultat :

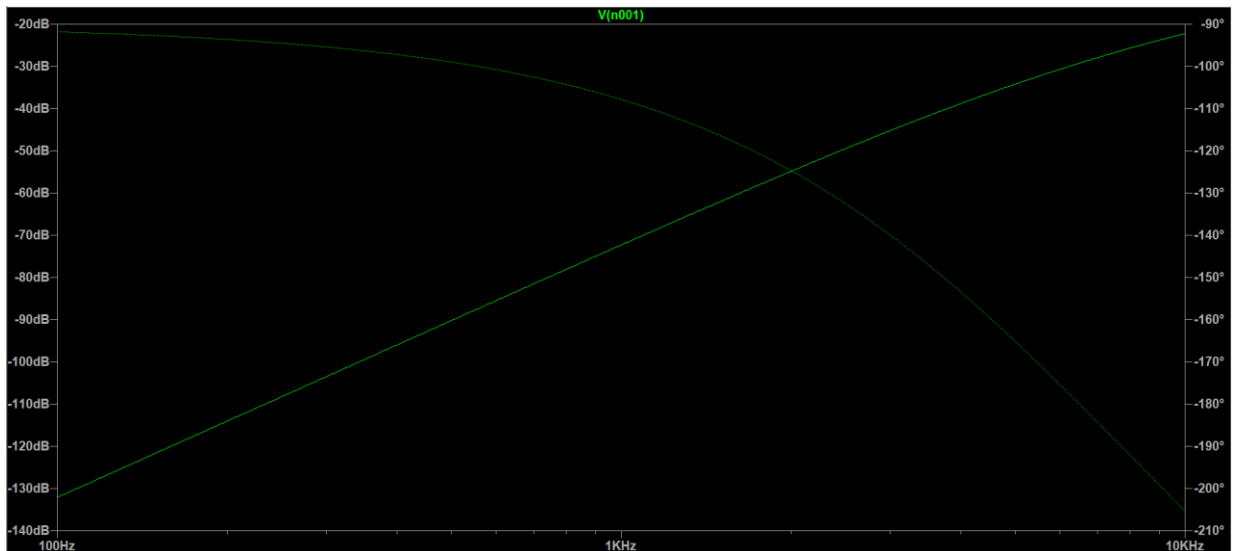

3. D'après la question 1 :

$$\beta(j\omega) = \frac{1}{1 - \left( \frac{5}{\omega^2 C^2 R^2} + \frac{6j}{\omega CR} - \frac{j}{\omega^3 C^3 R^3} \right)}$$


$$\varphi = -\arctan \frac{6(\omega CR)^2 - 1}{(\omega CR)^3 - 5\omega CR} = -\pi$$

$$\omega_0 = \frac{1}{\sqrt{6}CR}$$

$$|\beta(j\omega)|_{\omega=\omega_0} = \frac{1}{29}$$

$$A = \frac{1}{|\beta|} = 29$$
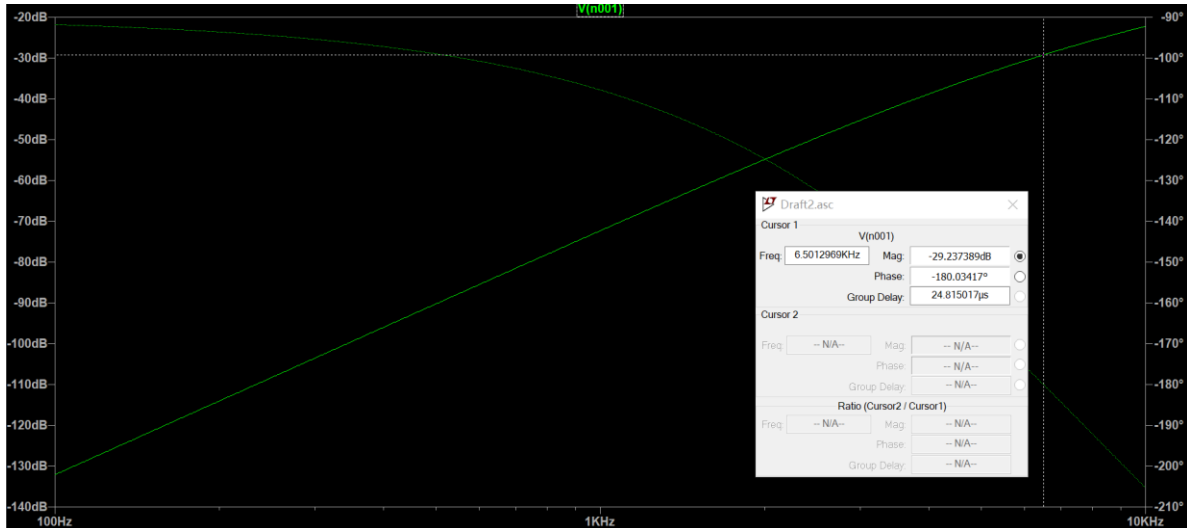
$$f_0 = \frac{1}{2\pi\sqrt{6}RC} = 6497.5\text{Hz}$$




On peut voir que  $A = -29.24$

$$f_0 = 6501.3\text{Hz}$$

4. La stabilité est définie par :

$$S(\omega_0) = \left| \frac{d\varphi(\beta(j\omega))}{d(\omega/\omega_0)} \right|_{\omega=\omega_0}$$

$$\text{Donc, } S(\omega_0) = \left| -\frac{12}{(\omega_0 CR)^2 - 5} \times \omega_0 CR \right| = \frac{12\sqrt{6}}{29} \approx 1.01$$

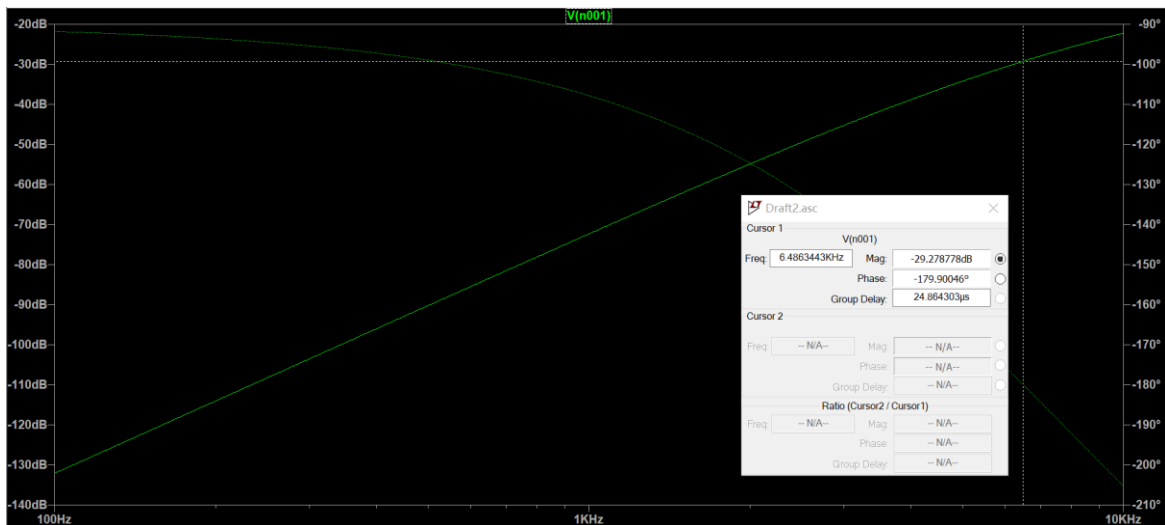


Donc,


$$S(\omega_0) = \left| \frac{d\varphi(\beta(j\omega))}{d(\omega/\omega_0)} \right|_{\omega=\omega_0} = \left| \frac{d\varphi(\beta(j\omega))}{d\omega} \omega_0 \right|_{\omega=\omega_0} =$$

$$\left| \frac{d\varphi(\beta(j\omega))}{df} \frac{\omega_0}{2\pi} \right|_{\omega=\omega_0} = \left| \frac{(180.03417^\circ - 179.90046^\circ) / 180^\circ \times \pi}{6501.3 - 6486.3} \frac{\omega_0}{2\pi} \right|_{\omega=\omega_0} \approx 1.011$$


5.

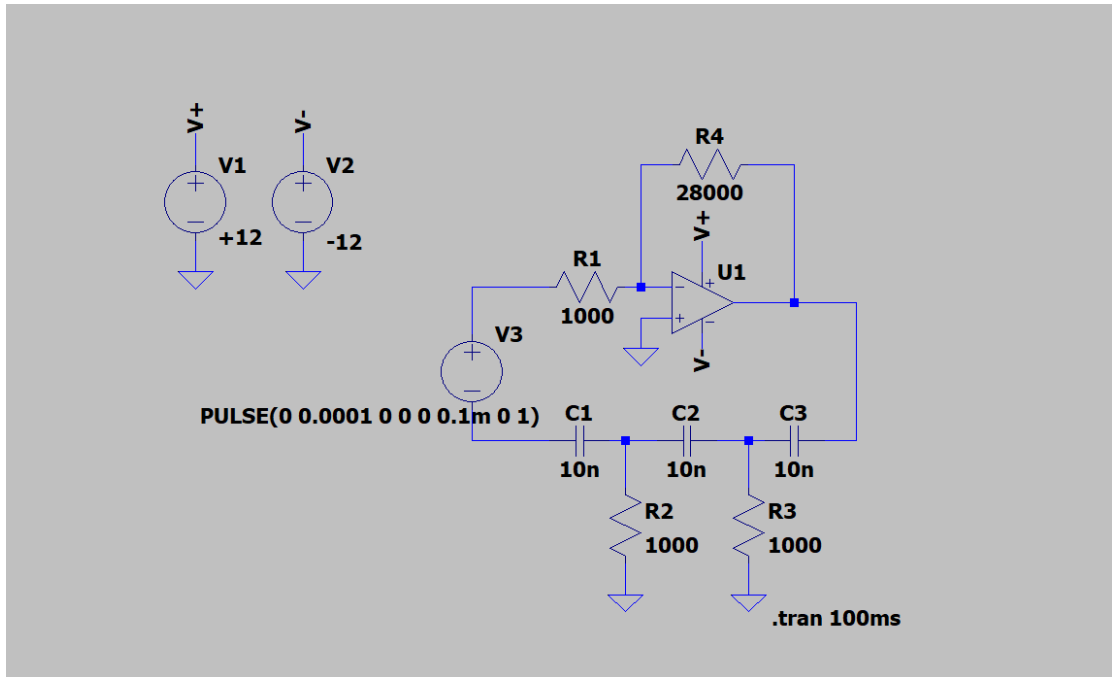

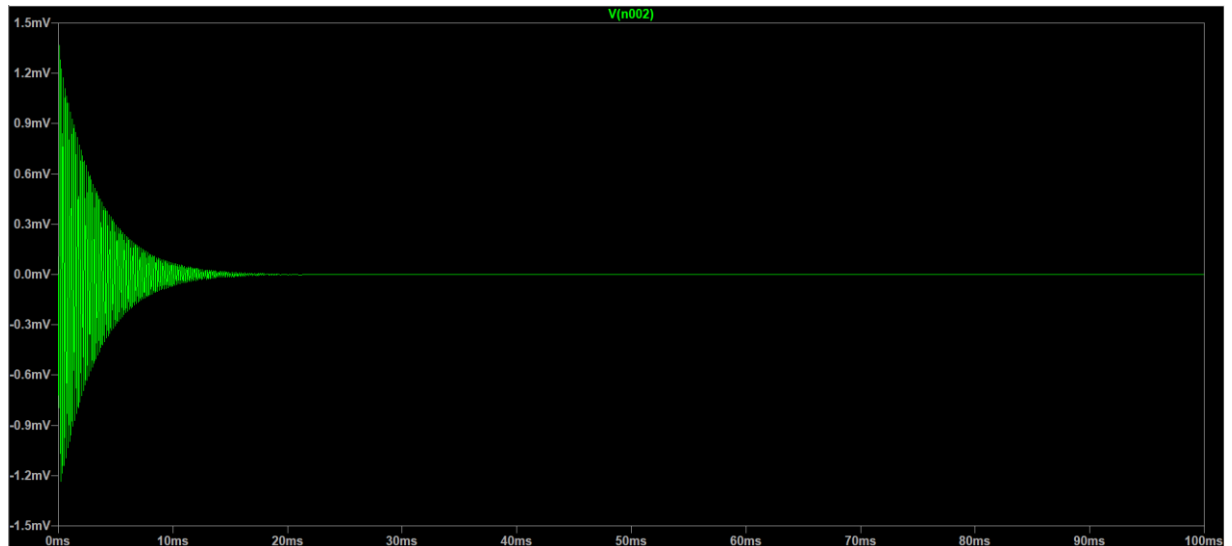
6. Quand on choisit  $R_2 = 28000\Omega$ ,  $A\beta < 1$ , on a :



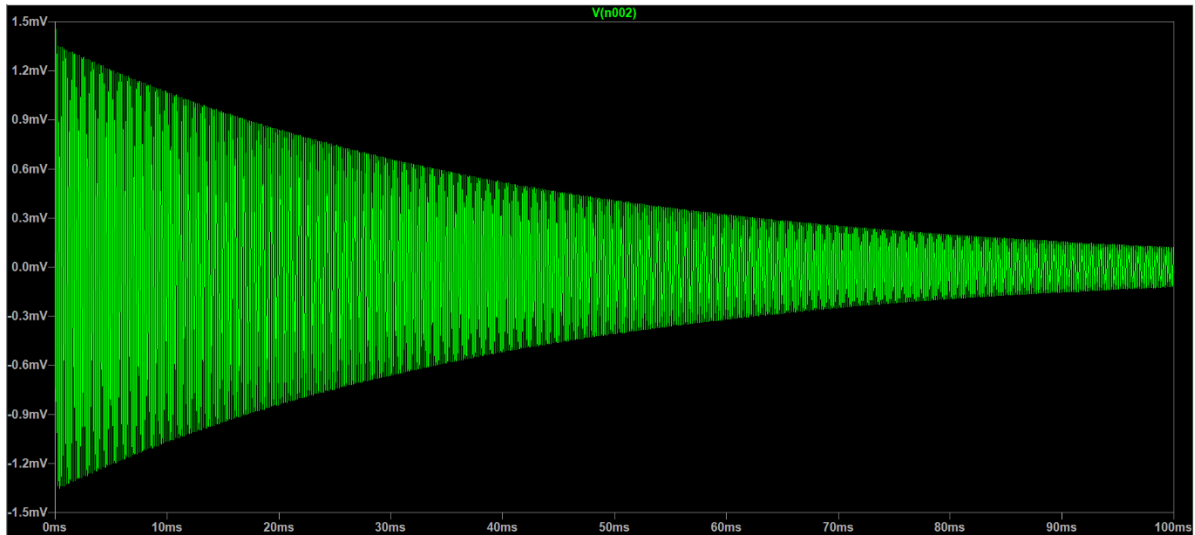
Quand on choisit  $R_2 = 29000\Omega$ ,  $A\beta = 1$ , on a :



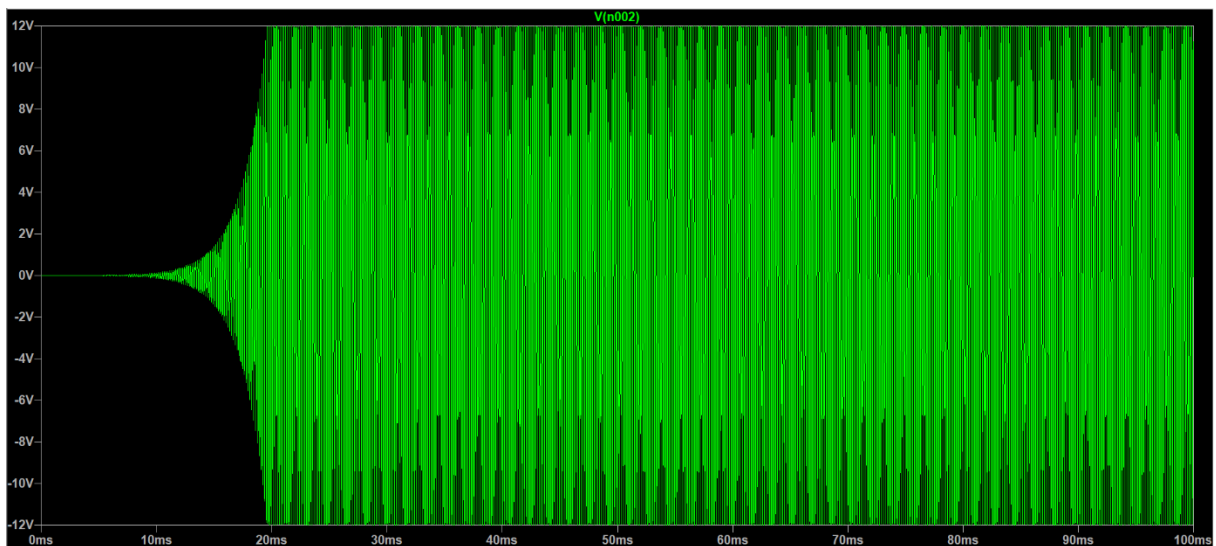
Quand on choisit  $R_2 = 31000\Omega$ ,  $A\beta > 1$ , on a :



7.

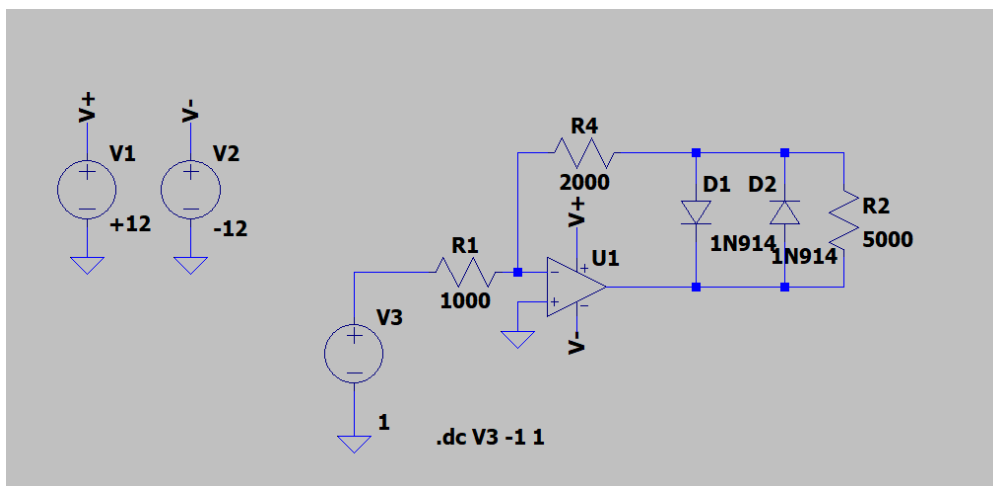

8.

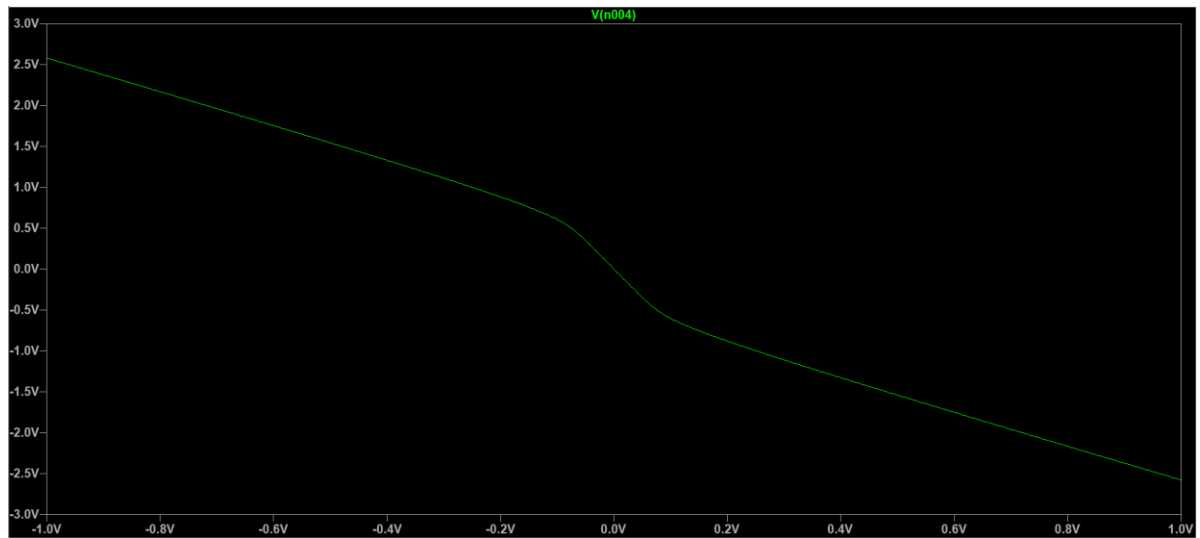

Il apparaît la non-linéarité du gain introduite par les diodes.